

# Syllabus

## Unit - I

### Introduction to Electrical Circuits

- \* Basic definitions
- \* Kirchhoff's Law's
- \* Series & Parallel connection
- \* Source transformation
- \* Mesh Analysis
- \* Nodal Analysis
- \* star to Delta and Delta to star transformation

## UNIT - II

### DC theorems and Single phase AC circuits

#### PART - A DC Theorems

- \* Super-position theorem
- \* Reciprocity theorem
- \* Thevenins theorem
- \* Norton's theorem
- \* Maximum power transfer Theorem

#### PART-B Single phase AC circuits

- \* Basic definitions
- \* AC through series RL, RC, RLC
- \* Problems

## UNIT - III

### Three phase AC circuits and PN junction diode

#### PART-A Three phase AC circuits

- \* Basic definitions
- \* Three phase star connection system and Three phase Delta connection system.


## PART-B P-N Junction diode

- \* Introduction
- \* V-I characteristics
- \* Ideal vs Practical diodes
- \* Effect of temperature on diode

## UNIT-IV Rectifiers and Special purpose devices
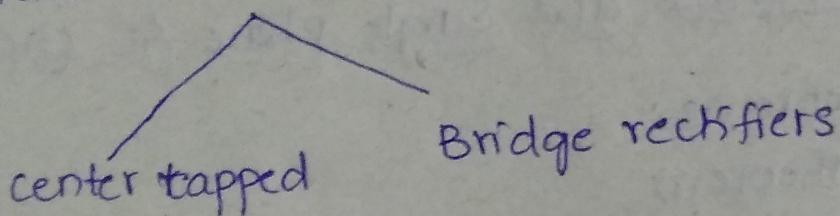
### PART-A Rectifiers

- \* Half wave rectifiers
- \* Full wave rectifiers



### PART-B Special purpose devices

- \* Break down mechanisms
- \* Zener diode characteristics
- \* Zener diode as voltage regulator


## UNIT-V Bipolar Junction Transistor

- \* Basic definitions
- \* Transistor configurations
  - i) CB
  - ii) CE
  - iii) CC
- \* DC and AC load line
- \* Need for biasing and biasing techniques

# UNIT-I Introduction to Electrical Circuits

1. Network: A combination of various electrical elements connected in any manner in a closed path is known as network.
2. Circuit: A circuit is a closed path through which an electrical current flows.
3. Branch: It's a portion of network which lies between two nodes.
4. Node: It is a common point (or) junction point where two or more branches pass through it.
5. Loop: It's a closed path which is formed by branches and nodes.
6. Mesh: It is a type of loop that doesn't contain another loop within it.

## Network elements

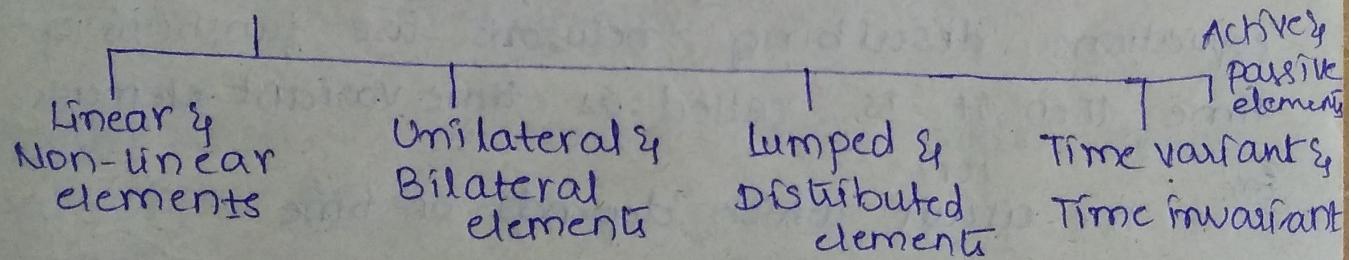

### Linear & Non-linear elements:

Linear: An element is said to be linear when it obeys Ohm's law  
Ex:- RLC

Non-linear: An element is said to be non-linear when it doesn't obey ohm's law  
Ex: Diodes, Transistors

Unilateral elements: The elements which allow the flow of current only in one direction, are called as Unilaterals.

Ex: Diodes, Metal rectifiers.

Bilateral elements: The elements which allow the flow of current in both the directions are called as bilateral elements.

Ex: RLC

Lumped elements: The elements which can be separated physically are called lumped elements.

Ex: Elements from mother board can be separated physically.

Distributed elements: The elements which cannot be separated physically.

Ex: The elements of transmission lines.

Time variant elements: If the coefficients of differential equations describing network are functions of time then it is called as time variant elements.

Ex: The circuit which depends on time  
(or)

Ex: The circuits devices which are designed with a speed limit.

Time invariant elements: If the coefficients of differential equations describing network are constant.

Ex: Working of RLC.

Active elements: The elements which can produce (or) generate energy are called active elements. We have two kinds of active elements they are current source and voltage source.

Ex:- Generators, Transistors

Passive elements: The elements which consumes or stores energy

Ex:- RLC

Linear circuit: The circuit which obeys the Ohm's law.

Non-linear circuit: The circuit which doesn't obey Ohm's law.

Source: The element (or) component producer energy.

Ex: battery, generators, RPS.

Load: The load is a component which consumer energy and converts electrical energy into other forms of energy.

Ex: fans, lights, refrigerator

Switch: It is a mechanical device which makes and breaks the circuit.

current  
circuit: The rate of change of charge with respect to time.

$$I = \frac{q}{t}$$

Units: columbs/sec (or) Amperes (A)

Voltage: The potential difference between any two points.

$$V = IR$$

R - proportionality constant

Units: Volts

Power: The workdone with respect to time.

$$P = \frac{W}{t}$$


Units: Jouls/sec (or) Watts

Resistance: The property of opposing the flow of current is called resistance.

$$R = \frac{V}{I}$$


Units:  $\Omega$  (ohm's)

Symbol:

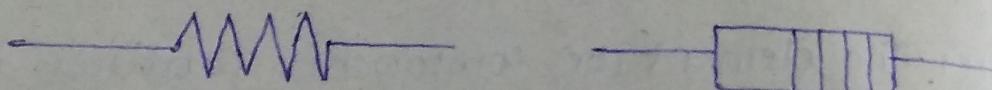

Inductor: Inductor is a coil which stores energy in the form of magnetic field.

Symbol:

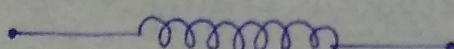


Units: Henry's

$$V = I \times \frac{dI}{dT}$$

Capacitor: It stores the energy in the form of electrical charge

Symbol:

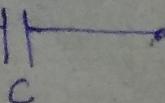

$$I = C \times \frac{dV}{dt}$$

Units: Farad's.

Ohm's Law: At constant temperature, the applied voltage is directly proportional to the current.

$$V = IR$$

$$R = \frac{V}{I}$$

$$I = \frac{V}{R}$$

### Limitations of Ohm's law:

1. It can't be applied for varying temperatures.
2. It can't be applied for unilateral elements.
3. It can't be applied for non-linear circuits.
4. It can't be applied for the semiconductors.


### Kirchhoff's laws:

These laws are used to solve complex networks. It tells about the voltage and current relationships in circuit. There are two laws they are:

① Kirchhoff's Voltage Law

② Kirchhoff's Current Law

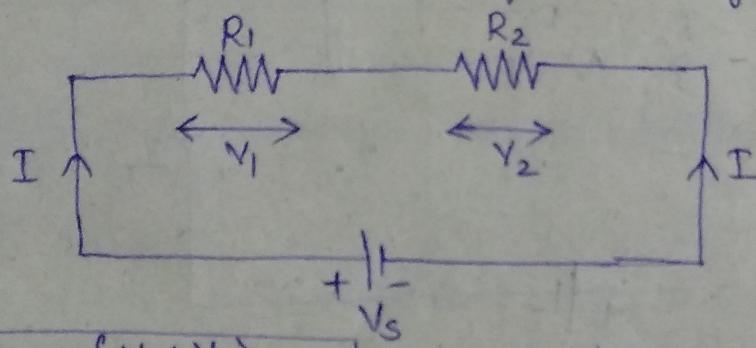① Kirchhoff's Voltage Law: The algebraic sum of voltage applied and voltage drops around a closed path in a network is equal to zero.



$$Vs = (V_1 + V_2) = 0$$

(or)

The applied voltage will be equal to the sum of voltage drops around a closed path.


$$Vs = V_1 + V_2$$

\* KVL is based on law of conservation of energy.

② Kirchhoff's Voltage Current law: The algebraic sum of currents at a node is equal to zero.


$$\sum I_n = 0$$

$$I_1 + I_3 + I_5 - I_2 - I_4 = 0$$

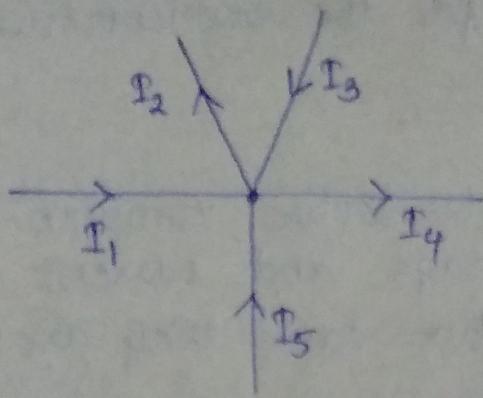


The sum of entering currents is equal to sum of leaving currents.


$$I_1 + I_3 + I_5 = I_2 + I_4$$

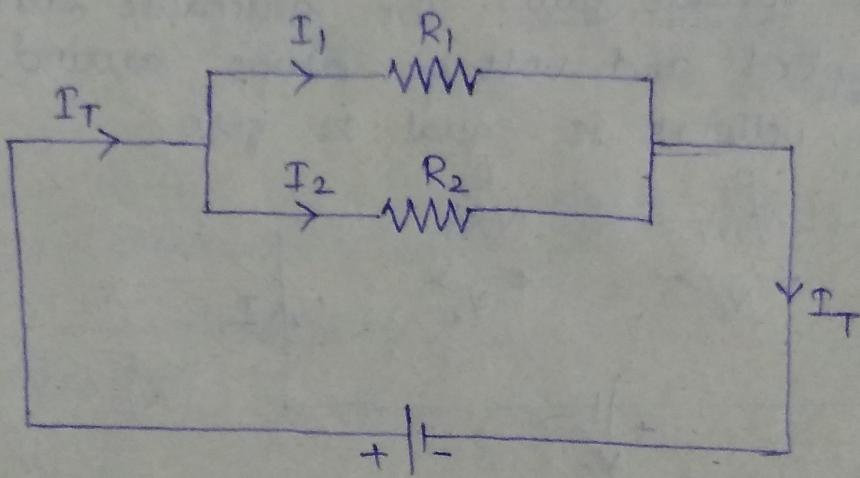

\* It is based on the Law of Conservation of charges.

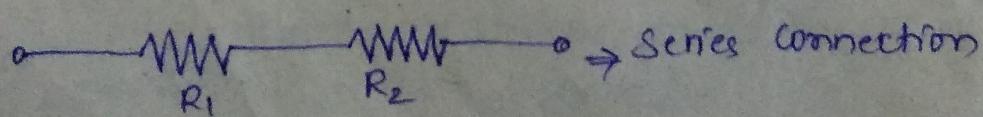Series Connection: If the resistors are connected end-to-end then the combination (or) connection is said to be in Series.



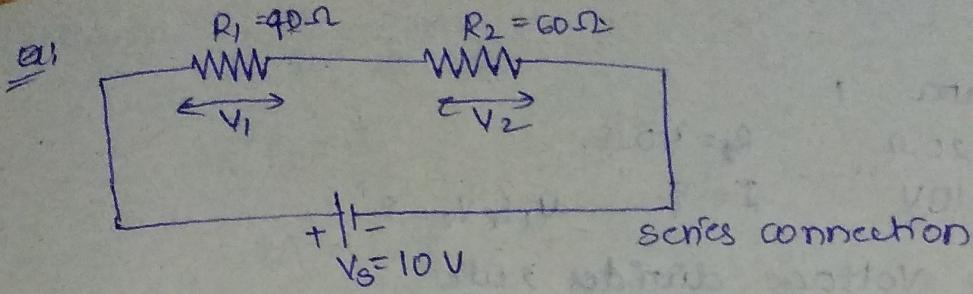


find the flow of current ( $I$ )?

$$[V \propto I] \quad V = IR$$

$$I = \frac{V}{R_{eq}} = \frac{10}{100} = 0.1 \text{ A}$$

$$R_{eq} = R_1 + R_2 + \dots$$

Voltage division / divider Rule:

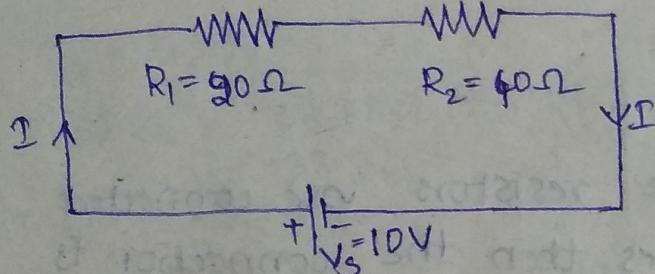

$$[V = IR]$$

$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

Calculate the voltage drops from the circuit

(b)  $V_1 = ?$  &  $V_2 = ?$

Method:

Given data

$$R_1 = 20\Omega \quad R_2 = 40\Omega$$

$$V_s = 10V \quad I = ? \quad V_1 \text{ & } V_2 = ?$$

$$I = \frac{V}{R_{eq}}$$

$$= \frac{10}{20+40} = \frac{10}{60} \text{ A}$$

$$V_1 = IR_1$$

$$= \left(\frac{10}{60}\right) \times 20 = 3.3V$$

$$V_2 = IR_2$$

$$= \left(\frac{10}{60}\right) \times 40 = 6.6V$$

$$V_s = V_1 + V_2$$

$$10 = 3.3 + 6.6$$

## II method

① Given data

$$R_1 = 20 \Omega \quad R_2 = 40 \Omega$$

$$V_S = 10V \quad I = ? \quad V_1, V_2 = ?$$

According to Voltage divider rule

$$V_1 = \frac{R_1}{R_{eq}} V_S$$

$$R_{eq} = R_1 + R_2 \\ = 20 + 40 \\ = 60 \Omega$$


$$= \frac{20}{60} \times 10 = 3.33V$$

$$V_2 = \frac{R_2}{R_{eq}} V_S$$


$$= \frac{40}{60} \times 10 = 6.66V$$

$$V_S = V_1 + V_2$$

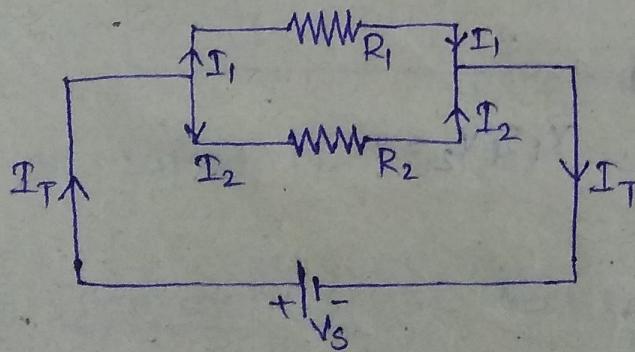Parallel Connection: If the resistors are connected through the common nodes then the connection is said to be parallel connection.



Ex:

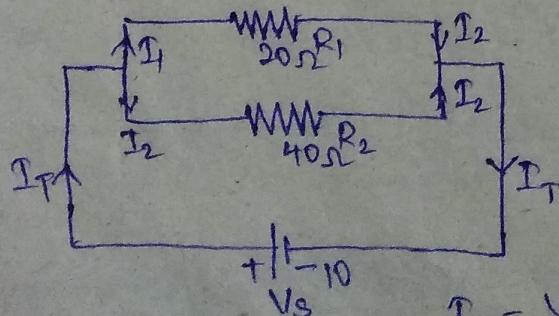

$$R_{eq} \text{ in } II \Rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$I_T = \frac{V_S}{R_{eq}}$$

$$I_1 = I_T \times \frac{\text{OPPR}}{\text{sum of } R}$$

$$I_2 = I_T \times \frac{\text{OPP}}{\text{sum of } R}$$

$$I_T = I_1 + I_2$$

$$\text{Req in parallel} \quad \frac{1}{R} = \frac{1}{20} + \frac{1}{40}$$

$$\frac{1}{R} = \frac{3}{40}$$

$$R = 0.075$$

$$I_T = \frac{10}{0.075} = 133.33$$

$$I_1 = 133.33 \times \frac{R_1}{R_1 + R_2}$$

$$I_1 = 88.88$$

$$I_2 = 133.33 \times \frac{R_2}{R_1 + R_2}$$

$$I_2 = 44.44$$

$$I_T = I_1 + I_2$$

$$133.33 = 88.88 + 44.44 \\ = 133.32$$

### Key points

\* When the two resistances are connected in parallel, its equivalent to

$$\boxed{\text{Req} = \frac{R_1 R_2}{R_1 + R_2}}$$

$$\text{Req in parallel}$$

$$\boxed{\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}}$$

\*  $I_1 = I_T \times \frac{\text{opposite resistance}}{\text{sum of resistances}}$ . This is the current flowing through resistance  $R_1$ , where  $I_T$  is total current

$$\boxed{I_T = \frac{V_s}{\text{Req}}}$$

\*  $I_2 = I_T \times \frac{\text{opposite resistance}}{\text{sum of resistances}}$ . This is the current flowing through resistance  $R_2$ .

\* When three resistances are connected in parallel

$$R_{eq} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$


$$(or) \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

\*  $I_1 = I_T \times \frac{R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$ . This is the current flowing through  $R_1$ , where  $I_T$  is total current  $I_T = \frac{V_s}{R_{eq}}$


\*  $I_2 = I_T \times \frac{R_1 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$ . This is the current through  $R_2$ .

\*  $I_3 = I_T \times \frac{R_1 R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1}$ . This is the current through  $R_3$ .

Ex:

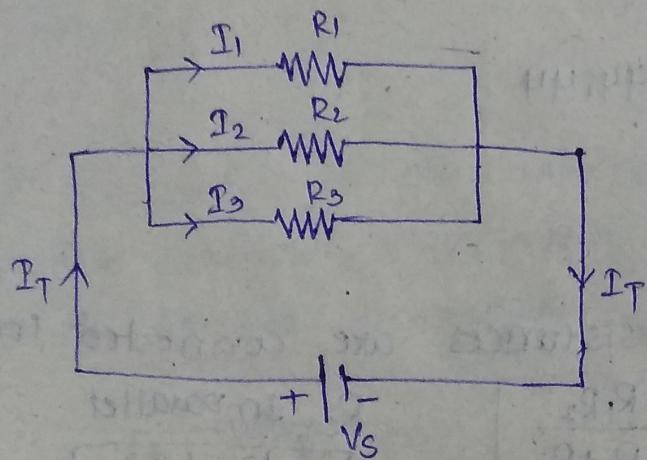

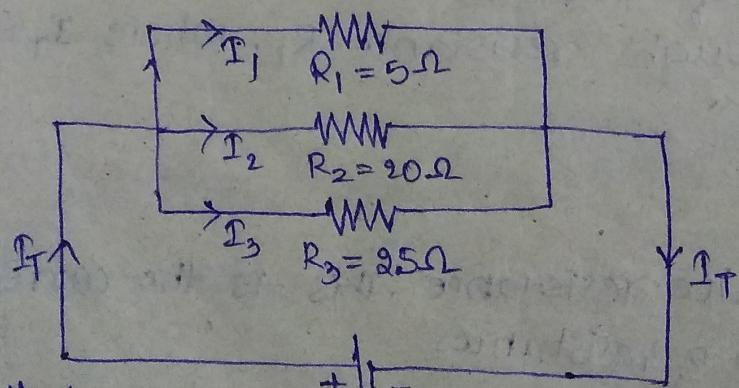Q. Calculate the total current and branch currents for the following circuit.



Given that  $V_s = 10V$

$$R_1 = 5$$

$$R_2 = 20$$

$$R_3 = 25$$

$$I_T, I_1, I_2, I_3 = ?$$

$$R_{eq} = \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3}$$

$$= 1.538 \Omega$$

$$I_T = \frac{V_s}{R_{eq}}$$

$$I_T = \frac{10}{1.538} A$$

$$= 6.501 A$$

from Ohm's law

$$(or) I_1 = \frac{V}{R_1} = \frac{10}{5} = 2A$$

$$I_1 = 6.501 \times \frac{20 \times 2.5}{5 \times 20 + 20 \times 2.5 + 2.5 \times 5}$$

$$\boxed{I_1 = 2.002 A}$$

from Ohm's law

$$I_2 = 6.501 \times \frac{2.5 \times 5 \times 2.5}{5 \times 20 + 20 \times 2.5 + 2.5 \times 5} \quad (or) \quad I_2 = \frac{V}{R_2} = \frac{10}{20} = \frac{1}{2} = 0.5A$$

$$\boxed{I_2 = 0.5A}$$

$$I_3 = 6.501 \times \frac{20 \times 5}{5 \times 20 + 20 \times 2.5 + 2.5 \times 5} \quad (or) \quad \text{from Ohm's law} \quad I_3 = \frac{V}{R_3} = \frac{10}{2.5} = 4A$$

$$\boxed{I_3 = 4A}$$

Sum of incoming i = Sum of outgoing i (current)

$$6.501 = 2.002 + 0.5 + 4$$


$$6.501 \approx 6.502$$

$$U.S = R.H.S$$
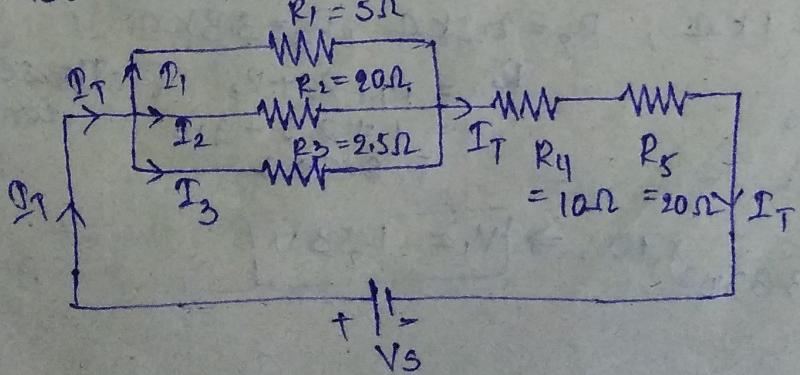
### Series-Parallel connection:

The connection which combines the characteristics of series and parallel circuit or connection.

It is also called a combinational circuit.




Q: Calculate the Req in the above circuit  
 Given data  
 $R_1 = 5\Omega$   $R_2 = 20\Omega$   $R_3 = 2\Omega$   
 $R_4 = 10\Omega$   $R_5 = 20\Omega$   
 $Req = ?$

Req of  $\Pi$  connection

$$Req = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$Req = 1.538\Omega$$


Series:

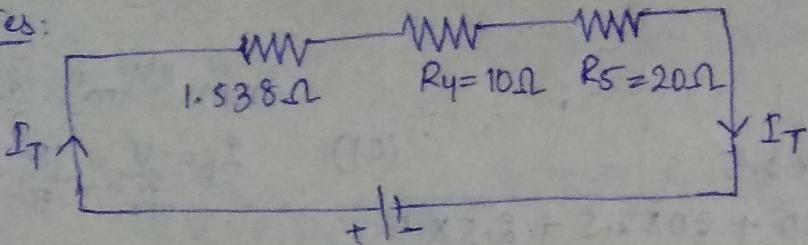

Now the circuit is connected in series connection.

$$\begin{aligned} Req_{ser} &= 1.538\Omega + R_4 + R_5 \\ &= 1.538\Omega + 10\Omega + 20\Omega \end{aligned}$$

$$Req = 31.538\Omega$$

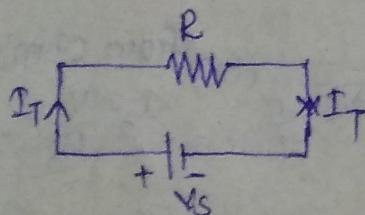


The total resistance across the circuit is  $31.538\Omega$

### ① KVL

$$R_1 = 1k\Omega \quad R_2 = 2.2k\Omega \quad R_3 = 3.3k\Omega$$

Given

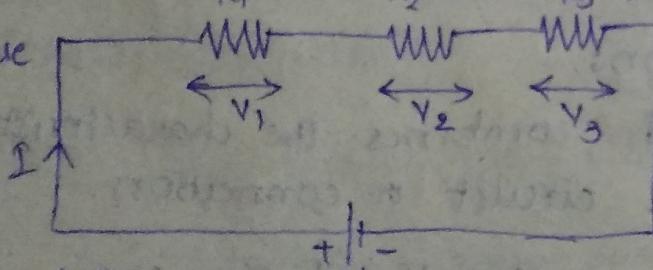

Given data

$$V_s = 10V, R_1 = 1k\Omega, R_2 = 2.2k\Omega, R_3 = 3.3k\Omega$$

$$V_1 = \frac{R_1}{Req} \times V_s$$

$$\begin{aligned} Req &= R_1 + R_2 + R_3 \quad [ \because \text{It's a series connection} ] \\ &= 1 + 2.2 + 3.3 \\ &= 6.5k\Omega \end{aligned}$$

$$= \frac{1 \times 10^3}{(1+2.2+3.3) \times 10^3} \times 10 \Rightarrow V_1 = 1.53V$$

$$V_2 = \frac{R_2}{R_{eq}} \times V_s$$

$$= \frac{2.2 \times 10^3}{(6.5) \times 10^3} \times 10$$

$$\boxed{V_2 = 3.38 \text{ V}}$$

$$V_3 = \frac{R_3}{R_{eq}} \times V_s$$

$$= \frac{3.3 \times 10^3}{(6.5) \times 10^3} \times 10$$

$$\boxed{V_3 = 5.07 \text{ V}}$$

$$V_s = V_1 + V_2 + V_3$$


$$10\text{V} = 1.53 + 3.38 + 5.07$$

$$10\text{V} \approx \underline{\underline{9.98\text{V}}}$$

②

### KCL

case(i)

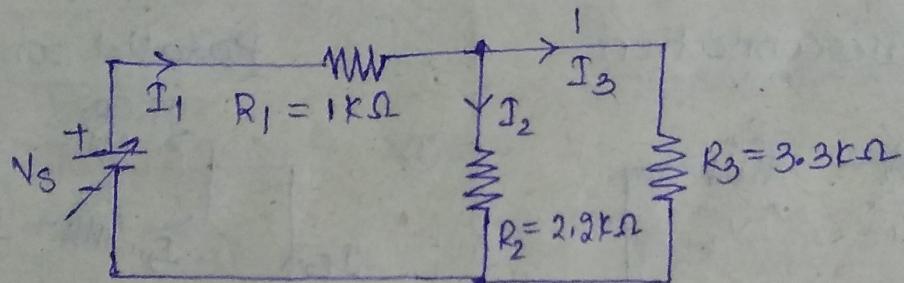

Given data

$$R_1 = 1\text{ k}\Omega$$




$$R_2 = 2.2\text{ k}\Omega$$

$$R_3 = 3.3\text{ k}\Omega$$

$$I_T \in I_1, I_2, I_3 = ?$$

$$R_{eq} = R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3} = \frac{2.2 \times 3.3 \text{ k}\Omega}{5.5 \text{ k}\Omega}$$

$$= 1.32 \text{ k}\Omega$$

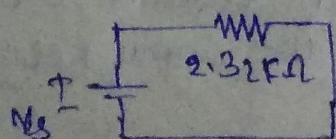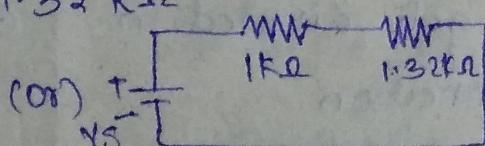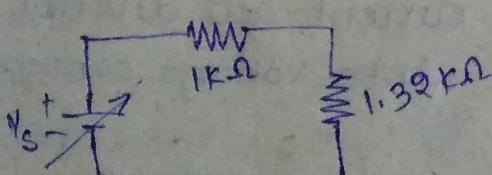

$$R_{eq} = 1\text{ k}\Omega + 1.32\text{ k}\Omega$$

$$= 2.32\text{ k}\Omega$$

$$\Rightarrow I_1 \text{ or } I_T = \frac{V_S}{R_{eq}} = \frac{10}{2.32 \times 10^3} = [4.31 \text{ mA} = I_T \text{ or } I_1]$$

$$\Rightarrow I_2 = \frac{I_T \times \text{OPPR}}{\text{sum of R}} = 4.31 \times \frac{3.3 \times 10^3}{2.2 \times 10^3 + 3.3 \times 10^3}$$

$$I_2 = 2.586 \text{ mA}$$

$$\Rightarrow I_3 = \frac{4.31 \times 2.2 \times 10^3}{(2.2 \times 10^3 + 3.3 \times 10^3)}$$

$$I_3 = 1.724 \text{ mA}$$

sum of incoming currents = sum of leaving currents


$$I_1 = I_2 + I_3$$

$$4.31 = 2.586 + 1.724$$


$$4.31 \text{ mA} = 4.31 \text{ mA}$$

### Differences between Series & Parallel connection

#### Series connection

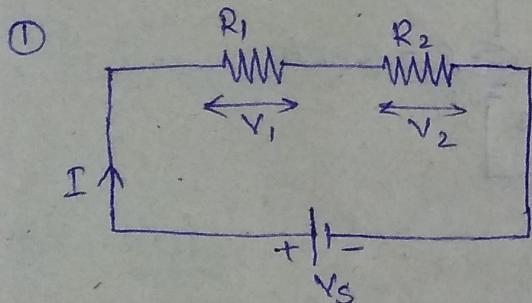

#### Parallel connection

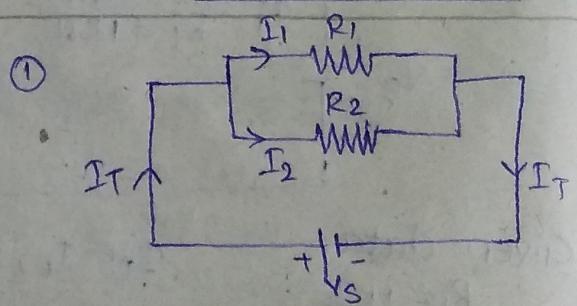

② Current (I) is constant in series connection.

② Voltage (V) is constant in parallel connection

③ Voltage gets divided in series connection

③ Current gets divided into voltage connection

④ In series connection, we apply KVL

④ In parallel connection, we apply KCL

⑤ The applied voltage is equal to sum of voltage drops around a closed path.

$$⑥ V_s = V_1 + V_2$$

$$⑦ V_1 = \frac{R_1}{R_1 + R_2} V_s \quad (\text{or}) \quad V_1 = I R_1$$


⑤ The sum of incoming currents is equals to sum of outgoing currents.

$$⑥ I_T = I_1 + I_2$$

$$⑦ I_1 = I_T \times \frac{\text{opp R}}{\text{sum of R}} \quad (\text{or})$$

$$I_1 = \frac{V_s}{R_1}$$

D calculate  $R_{eq}$

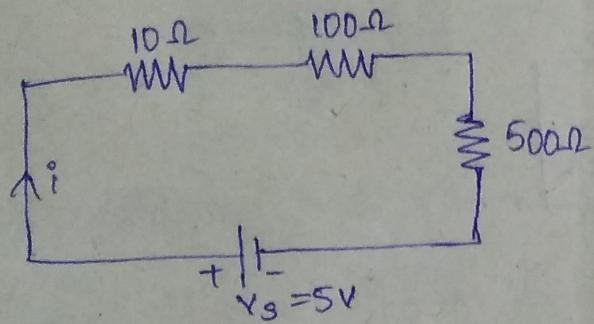


Given data

$$R_1 = 10\Omega, R_2 = 100\Omega, R_3 = 500\Omega$$

$$V_s = 5V$$

$$R_{eq} = R_1 + R_2 + R_3$$
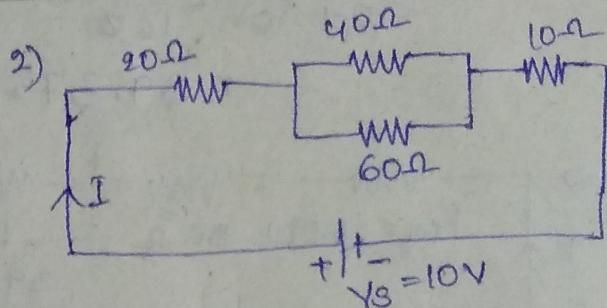
$$R_{eq} = 10 + 100 + 500 \\ = 610\Omega$$





Given data

$$R_1 = 20\Omega, R_2 = 40\Omega, R_3 = 60\Omega \\ V_s = 10V \quad R_4 = 10\Omega$$

$R_{eq}$  of 1<sup>st</sup> connection
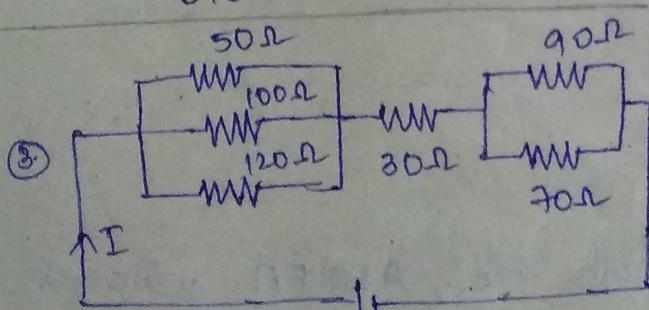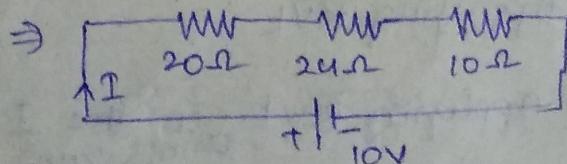
$$R_{eq} = \frac{R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} R_4 \\ = \frac{40 \times 60}{20 \times 40 + 40 \times 60 + 60} \times 10 \\ = \frac{40 \times 60}{1000} = 24\Omega$$



Given data  $V_s = 10V$

$$R_1 = 50\Omega$$

$$R_5 = 90\Omega$$

$$R_2 = 100\Omega$$


$$R_6 = 70\Omega$$

$$R_3 = 120\Omega$$

$$R_4 = 30\Omega$$

$$R_{eq} = R_1 + R_2 + R_3$$
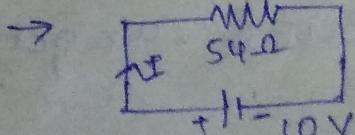
$$R_{eq} = 50 + 100 + 120 \\ = 270\Omega$$



Req of I<sub>II</sub> connection

$$Req = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$= \frac{50 + 100 + 120}{50 \times 100 + 100 \times 120 + 120 \times 50} \\ = 26.086$$

Req of 2nd U connection



$$Req = \frac{R_5 R_6}{R_5 + R_6}$$

$$= \frac{90 \times 70}{90 + 70} = \frac{6300}{160} \\ = 39.375$$

Req of Series connection


$$Req = R_1 + R_2 + R_3 \\ = 26.086 + 30 + 39.375$$

$$Req = \underline{\underline{95.46}}$$

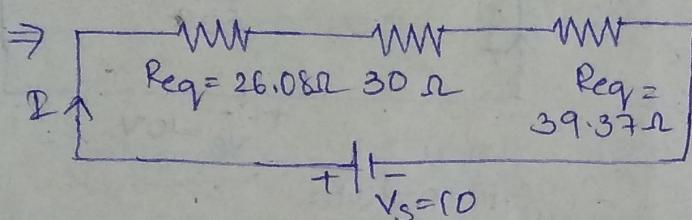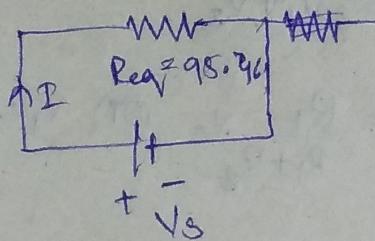

Mesh Analysis :-

①

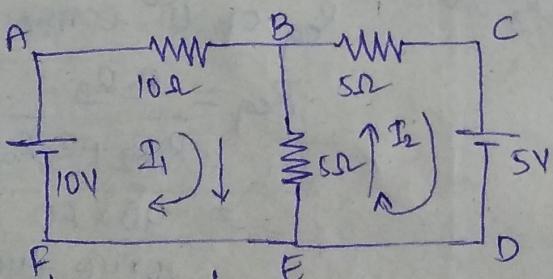

Steps to solve mesh:

- 1) Identify no. of meshes
- 2) No. of meshes = No. of i
- 3) Applying KVL
- 4) Solve equations

By Applying KVL to the I mesh i.e., ABEFA, we get

$$\Rightarrow 10V = 10I_1 + 5(I_1 - I_2)$$

$$\Rightarrow 10 = 15I_1 - 5I_2 \rightarrow ①$$

By applying KVL to the II mesh i.e., BCDEB, we get

$$\Rightarrow -5 = 5I_2 + 5(I_2 - I_1)$$

$$\Rightarrow -5 = -5I_1 + 10I_2 \rightarrow ②$$

by solving ① & ②


$$\text{we get } I_1 = 0.6 \text{ A} = I_{10\Omega}$$

$$I_2 = -0.2 \text{ A} = I_{5\Omega}$$

$$I_{5\Omega} (\text{Middle mesh}) = I_1 - I_2 (\text{I mesh}) = 0.8 \text{ A}$$

$$= I_2 - I_1 (\text{II mesh}) = -0.8 \text{ A (opp)}$$

② Pgnosst

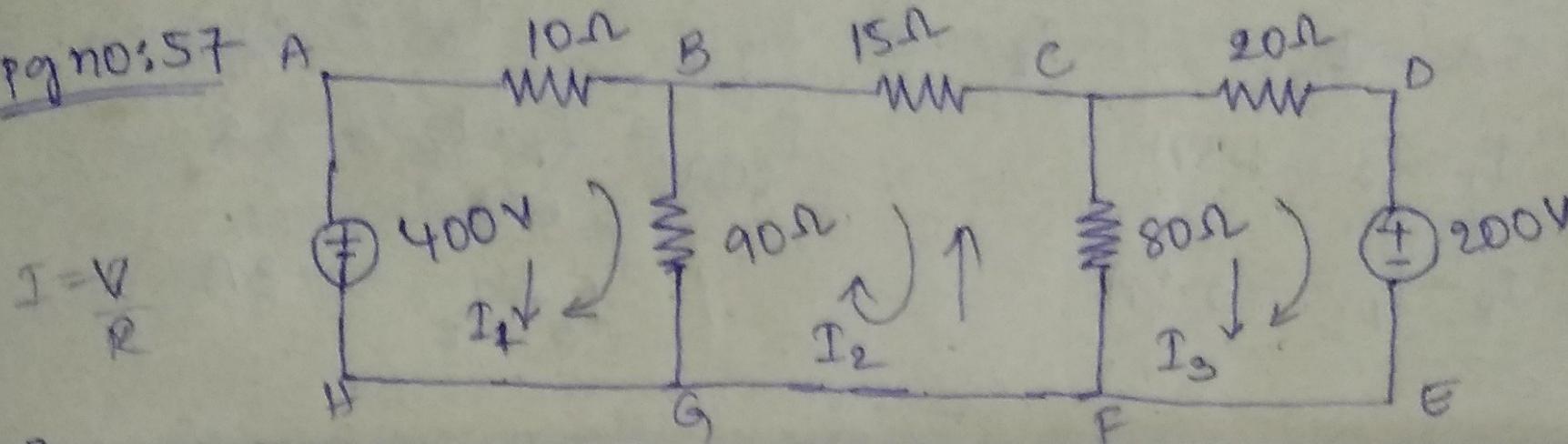

$$I = \frac{V}{R}$$

By applying KVL to 2nd mesh i.e., BCFG, we get

$$0 = 90(I_2 - I_1) + 15I_2 + 80(I_3 - I_2)$$

$$= 90I_2 - 90I_1 + 15I_2 + 80I_2 - 80I_3$$

$$0 = 185I_2 - 90I_1 - 80I_3 \quad \text{--- (1)}$$

By applying KVL to 3rd mesh i.e., CDEF, we get

$$-200 = 80(I_3 - I_2) + 20I_3$$

$$= 80I_3 - 80I_2 + 20I_3$$

$$-200 = -80I_2 + 100I_3 \quad \text{--- (2)}$$


By solving (1), (2) & (3) eqn's, we get

$$I_1 = 8.5A = I_{10\Omega} \quad I_2 = 5 = I_{15\Omega} \quad I_3 = 2 = I_{20\Omega}$$

$$I_{9\Omega} = I_1 - I_2 = 3.5A \quad I_{8\Omega} = I_2 - I_3 = 3A$$


$$I_2 - I_1 = -3.5A \quad I_3 - I_2 = -3A$$

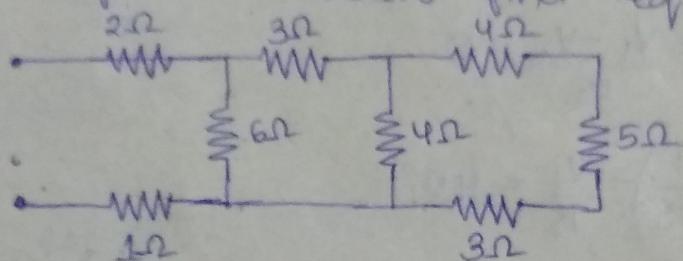\* By combining the resistors find  $R_{eq}$  (R equivalent)



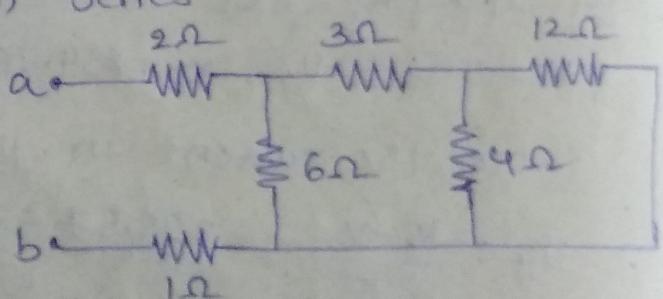
1)  $4\Omega$ ,  $5\Omega$  and  $3\Omega$  are in series

$$\begin{aligned} R_{eq} &= R_1 + R_2 + R_3 \\ &= 4 + 5 + 3 \\ &= 12\Omega \end{aligned}$$



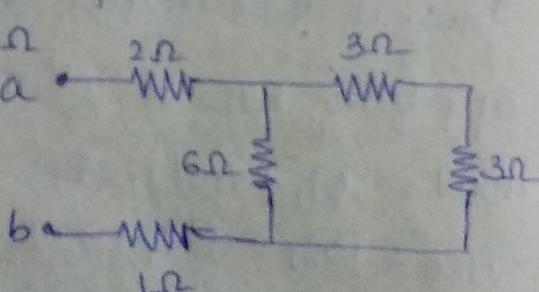
2)  $12\Omega$  and  $4\Omega$  are connected in parallel.

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{12 \times 4}{12 + 4} = \frac{48}{16} = 3\Omega$$



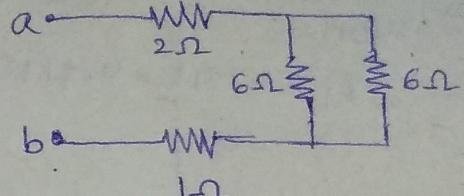
3)  $3\Omega$  and  $3\Omega$  are connected in series

$$R_{eq} = R_1 + R_2 \\ = 3 + 3 = 6\Omega$$



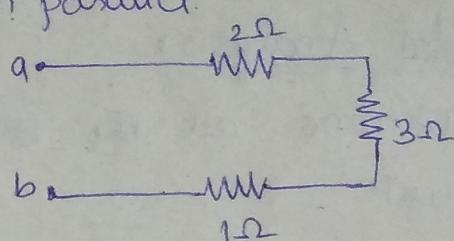
4)  $6\Omega$  &  $6\Omega$  are connected in parallel.

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \\ = \frac{6(6)}{6+6} = \frac{36}{12} = 3\Omega$$



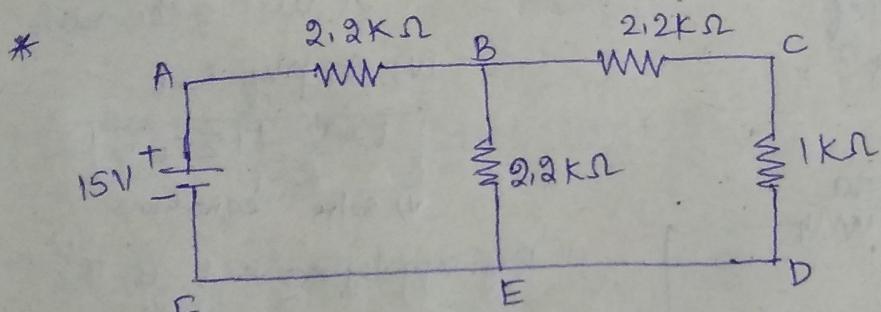5)  $2\Omega$ ,  $1\Omega$  and  $3\Omega$  are connected in series.

$$R_{eq} = R_1 + R_2 + R_3 \\ = 2 + 3 + 1 = 6\Omega$$



By using Mesh analysis determine current in all the branches.

By applying KVL to Mesh I i.e. ABEFA

$$15V = 2.2I_1 + 2.2(I_1 - I_2)$$

$$15 = 2.2I_1 + 2.2I_1 - 2.2I_2$$

$$15 = 4.4I_1 - 2.2I_2 \rightarrow ①$$

By applying KVL to Mesh II i.e. BCDEB

$$0 = 2.2I_2 + 2.2(I_2 - I_1) + 1(I_2)$$

$$0 = 2.2I_2 + 2.2I_2 - 2.2I_1 + I_2$$

$$0 = 4.4I_2 - 2.2I_1 + I_2$$

$$0 = 5.4I_2 - 2.2I_1 \rightarrow ②$$

By solving eqn ① & ②

$$I_1 = 4.281 \text{ mA} = I_{2.2k\Omega}$$

$$I_2 = 1.741 \text{ mA} = I_{2.2k\Omega}$$


$$I_{2.2k\Omega} = I_1 - I_2 = 4.281 - 1.741 = 2.54 \text{ mA}$$

(or)

$$I_2 - I_1 = 1.741 - 4.281 = -2.54 \text{ mA} \quad [I \text{ is in opp. direction}]$$
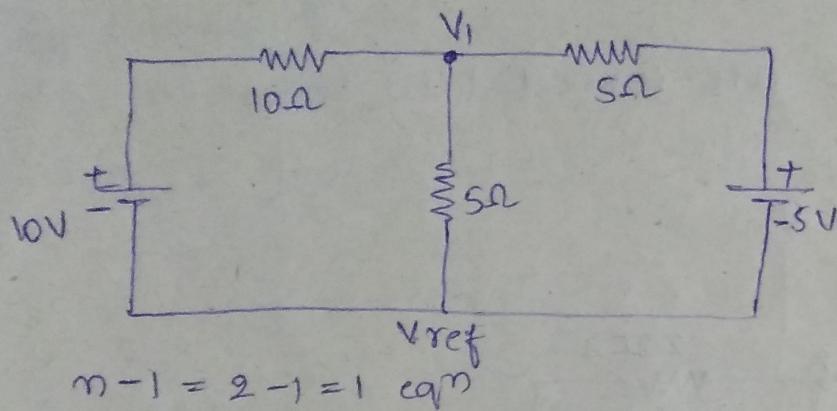
### Nodal Analysis:

- ① Determine all the branch currents using nodal analysis.



$$n-1 = 2-1 = 1 \text{ eqm}$$

i) Identify Principal nodes


ii) Redraw the circuit

iii) Assume all i leaving the node

iv) Apply KCL

$$i = \frac{V}{R} \quad \sum I = 0$$

v) Solve equations

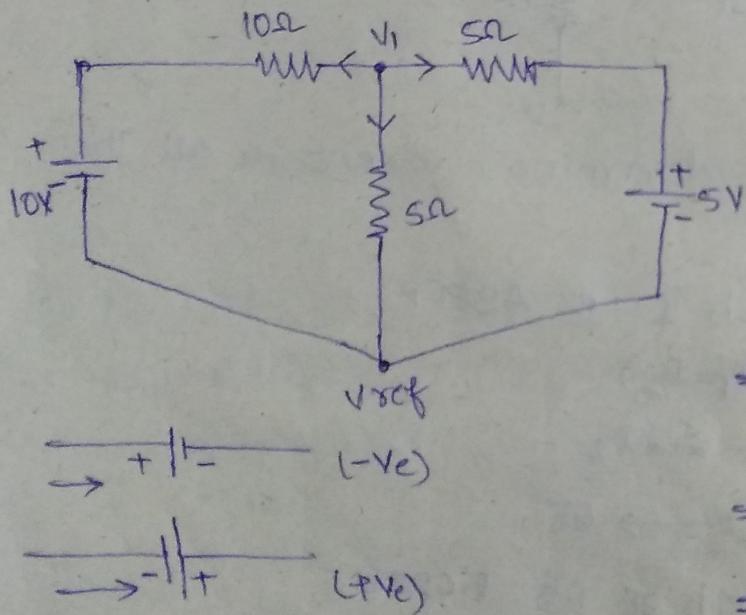

By applying KCL at the Principal node, we get

$$\Rightarrow \frac{V_1 - 10}{10} + \frac{V_1}{5} + \frac{V_1 - 5}{5} = 0$$

$$\Rightarrow \frac{V_1}{10} + \frac{V_1}{5} + \frac{V_1}{5} - \frac{10}{10} - \frac{5}{5} = 0$$

$$\Rightarrow V_1 \left( \frac{1}{10} + \frac{1}{5} + \frac{1}{5} \right) = 2$$


$$\Rightarrow V_1 (0.5) = 2$$

$$\Rightarrow \boxed{V_1 = 4 \text{ V}}$$

$$\Rightarrow I_{10\Omega} = \frac{V_1 - 10}{10} = \frac{4 - 10}{10} = -0.6 \text{ A}$$


$$\Rightarrow I_{5\Omega} = \frac{V_1}{5} = \frac{4}{5} = 0.8 \text{ A}$$
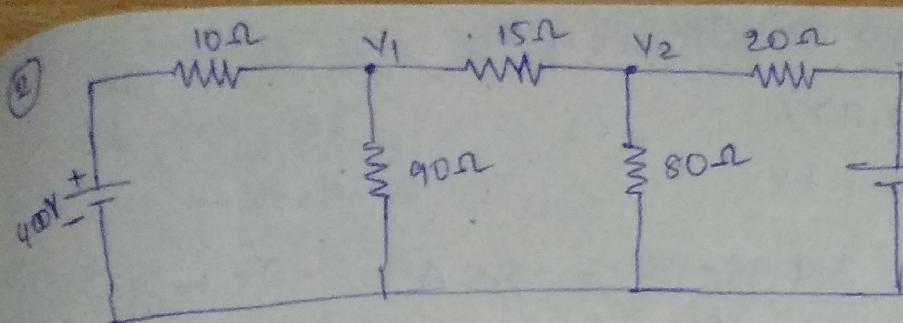
$$\Rightarrow I_{5\Omega} = \frac{V_1 - 5}{5} = \frac{4 - 5}{5} = -0.2 \text{ A}$$



Determine all  
the branch current  
using nodal  
analysis.

$$4-1=3-1=2 \text{ eqn } 3$$

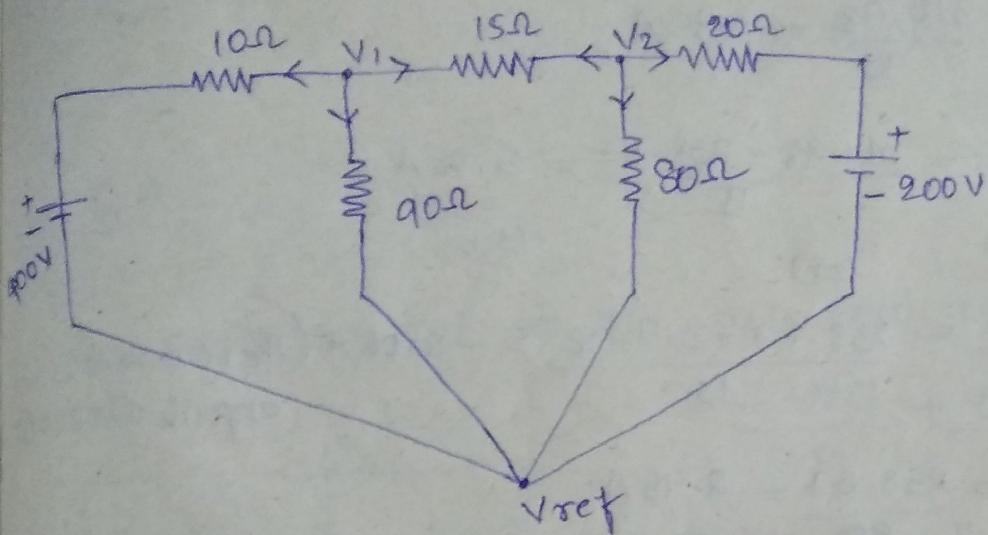

$$\Rightarrow \frac{V_1 - 400}{10} + \frac{V_1}{90} + \frac{V_1 - V_2}{15} = 0 \rightarrow ①$$

$$\Rightarrow \frac{V_2 - V_1}{15} + \frac{V_2}{80} + \frac{V_2 - 200}{20} = 0 \rightarrow ②$$

from ①

$$\frac{V_1}{10} + \frac{V_1}{90} + \frac{V_1}{15} - \frac{V_2}{15} - \frac{400}{10} = 0$$

$$V_1 \left( \frac{1}{10} + \frac{1}{90} + \frac{1}{15} \right) - \frac{V_2}{15} - 40 = 0$$

$$V_1 \left( \frac{8}{45} \right) - \frac{V_2}{15} - 40 = 0$$

$$V_1 (0.177) - \frac{V_2}{15} - 40 = 0 \Rightarrow V_1 (0.177) - V_2 \left( \frac{1}{15} \right) = 40$$

$$V_1 (0.177) - V_2 (0.066) = 40 - ①$$

from eqn ②

$$\frac{V_2}{15} - \frac{V_1}{15} + \frac{V_2}{80} + \frac{V_2}{20} - \frac{200}{20} = 0$$

$$V_2 \left( \frac{1}{15} + \frac{1}{80} + \frac{1}{20} \right) - \frac{V_1}{15} - 10 = 0$$

$$V_2 (0.129) - \frac{V_1}{15} - 10 = 0$$

$$V_2 (0.129) - V_1 \left( \frac{1}{15} \right) = 10$$

$$V_2 (0.129) - V_1 (0.066) = 10 - V_1 (0.066) + V_2 (0.129) = 10 - ②$$

By solving eqn ① & ②, we get

$$V_1 = 314.98 \text{ V}$$

$$V_2 = 238.67 \text{ V}$$

$$I_{10\Omega} = \frac{V_1 - 400}{10} = \frac{314.98 - 400}{10} = -8.5 \text{ A}$$

$$I_{90\Omega} = \frac{V_1}{90} = \frac{314.98}{90} = 3.49 \text{ A}$$

$$I_{15\Omega} = \frac{V_1 - V_2}{15} = \frac{314.98 - 238.67}{15} = 5.08 \text{ A}$$

(or)


$$\frac{V_2 - V_1}{15} = \frac{238.67 - 314.98}{15} = -5.08 \text{ A} \quad (\text{The current is in opposite direction})$$

$$I_{80\Omega} = \frac{V_2}{80} = \frac{238.67}{80} = 2.98 \text{ A}$$

$$I_{20\Omega} = \frac{V_2 - 200}{20} = \frac{238.67 - 200}{20} = 1.93 \text{ A}$$

③ Determine all the branch currents by using mesh and nodal analysis.

i) M.A      ii) N.A

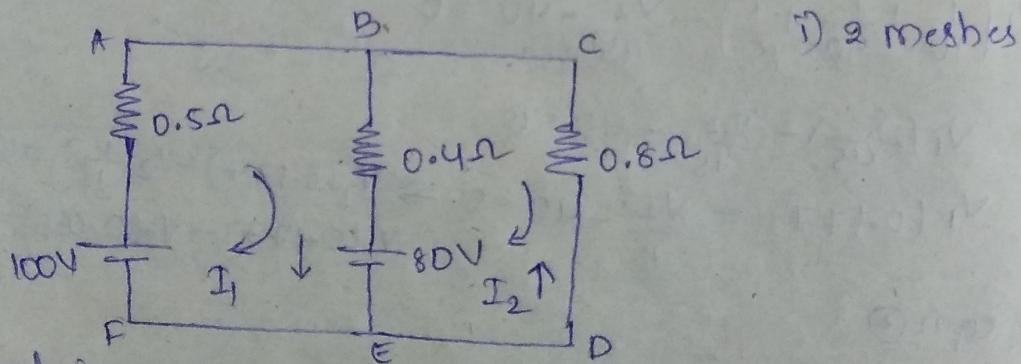

By applying KVL to the I mesh i.e., ABFEFA, we get

$$-80 + 100 \text{ V} = 0.5I_1 + 0.4(I_1 - I_2) \quad \text{--- ①}$$

$$20 \text{ V} = 0.5I_1 + 0.4I_1 - 0.4I_2 = 0.9I_1 - 0.4I_2$$

By applying KVL to the II mesh i.e., BCDEB, we get

$$\Rightarrow 80 \text{ V} = I_2(0.8) + 0.4(I_2 - I_1) \quad \text{--- ②}$$

$$= 0.8I_2 + 0.4I_2 - 0.4I_1$$

$$80 \text{ V} = 1.2I_2 - 0.4I_1$$

By solving ① & ②

we get

$$I_1 = 60.86 \text{ A} = I_{0.5\Omega}$$

$$I_2 = 86.95 \text{ A} = I_{0.4\Omega}$$


$$I_{0.4} (\text{Middle mesh}) = I_1 - I_2 (\text{I mesh}) = -26.09 \text{ (opp)}$$

$$= I_2 - I_1 (\text{II mesh}) = 26.09$$

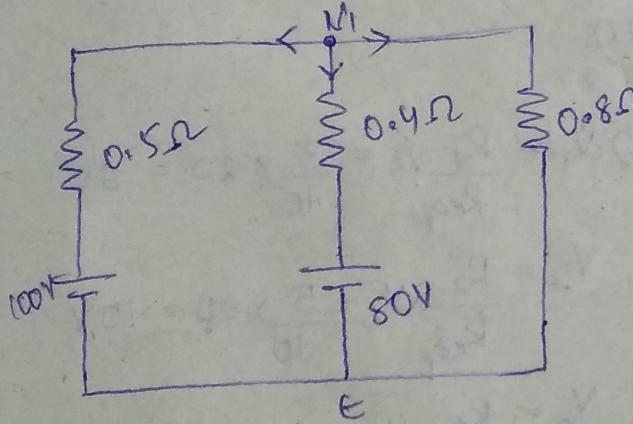(ii) N.A

$$m-1 = 2-1 = 1 \text{ eqn}$$

By applying KCL at the principal node i.e.,  $V_1$ , we get



$$\Rightarrow \frac{V_1 - 100}{0.5} + \frac{V_1 - 80}{0.4} + \frac{V_1}{0.8} = 0$$

$$\Rightarrow \frac{V_1}{0.5} - \frac{100}{0.5} + \frac{V_1}{0.4} - \frac{80}{0.4} + \frac{V_1}{0.8} = 0$$

$$\Rightarrow V_1 \left( \frac{1}{0.5} + \frac{1}{0.4} + \frac{1}{0.8} \right) = \left( \frac{100}{0.5} + \frac{80}{0.4} \right)$$

$$\Rightarrow V_1 (5.75) = 400$$

$$V_1 = 69.56 \text{ V}$$

Current across  $0.5\Omega$

$$I_{0.5\Omega} = \frac{V_1 - 100}{0.5} = -80.86 \text{ A} \text{ (opp)}$$

$$I_{0.4\Omega} = \frac{V_1 - 80}{0.4} = -26.1 \text{ A} \text{ (opp)}$$

$$I_{0.8\Omega} = \frac{V_1}{0.8} = 86.95 \text{ A}$$

22/5/22


HW problems

① For the circuit shown in fig. Determine the following.

(a) Equivalent resistance ( $R_{eq}$ )

(b) Current ( $I$ )

(c) Voltage drop across each resistor

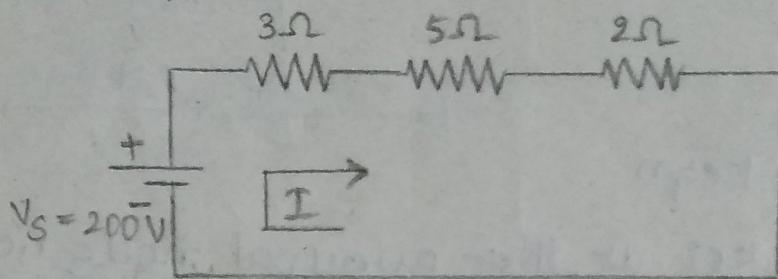

Sol:- Given data

$$R_1 = 3\Omega, R_2 = 5\Omega, R_3 = 2\Omega$$

$$V_s = 200V$$

$$\begin{aligned} (a) \quad R_{eq} &= R_1 + R_2 + R_3 \\ &= 3 + 5 + 2 \\ &= 10\Omega \end{aligned}$$

$$(b) \quad I = \frac{V_s}{R_{eq}} = \frac{20}{10} = 2A$$

$$(c) \quad V_1 = \frac{R_1}{R_{eq}} V_s = \frac{3}{10} \times 20 = 6V$$

$$V_2 = \frac{R_2}{R_{eq}} V_s = \frac{5}{10} \times 20 = 10V$$


$$V_3 = \frac{R_3}{R_{eq}} V_s = \frac{2}{10} \times 20 = 4V$$

② Determine the total amount of power in the series circuit and also find power across each resistance.

Sol:- Given data

$$R_1 = 10\Omega, R_2 = 4\Omega, R_3 = 6\Omega$$

$$V_s = 100V$$

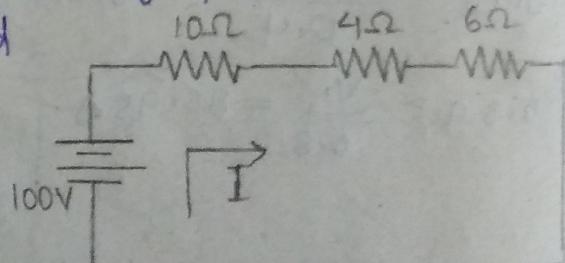

$$\begin{aligned} R_{eq} &= R_1 + R_2 + R_3 \\ &= 10 + 4 + 6 = 20\Omega \end{aligned}$$

$$I = \frac{V_s}{R_{eq}} = \frac{100}{20} = 5A$$

$$\begin{aligned} P_{\text{total}} &= V \times I \\ &= 100 \times 5 \\ &= \underline{\underline{500 \text{W}}} \end{aligned}$$

$$\left\{ \begin{array}{l} [P = V \times I] \\ P = I^2 R \quad [V = IR] \\ P = \frac{V^2}{R} \end{array} \right.$$

$$\begin{aligned} P_{10\Omega} &= I^2 R \\ &= (5)^2 \times 10 \end{aligned}$$

$$\boxed{P_{10\Omega} = 250 \text{W}}$$

$$\begin{aligned} P_{4\Omega} &= I^2 R \\ &= (5)^2 \times 4 \end{aligned}$$

$$\boxed{P_{4\Omega} = 100 \text{W}}$$

$$\begin{aligned} P_{6\Omega} &= I^2 R \\ &= (5)^2 \times 6 \end{aligned}$$

$$\boxed{P_{6\Omega} = 150 \text{W}}$$

⑤ For the circuit shown in figure determine the unknown voltage drop  $V_r$

Sol: Given data

$$V_s = 30 \text{V}, V_1 = 2 \text{V}, V_2 = 1 \text{V},$$

$$V_3 = 5 \text{V}, V_4 = 3 \text{V}, V_r = ?$$

According to KVL law


$$V_s = V_1 + V_2 + V_3 + V_r + V_4$$

$$30 = 2 + 1 + V_r + 5 + 3$$

$$30 = 11 + V_r$$

$$V_r = 30 - 11$$

$$\boxed{V_r = 19 \text{V}}$$


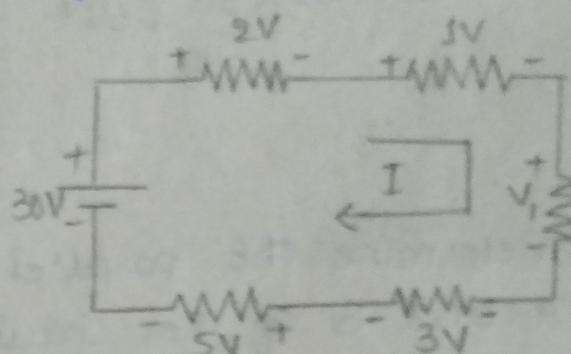


⑥ In the circuit given in figure find (a) the current, and (b) the voltage across  $30\Omega$

Sol: Given data

$$R_1 = 8\Omega, R_2 = 30\Omega, R_3 = 2\Omega$$

$$V_s = 30 \text{V}$$

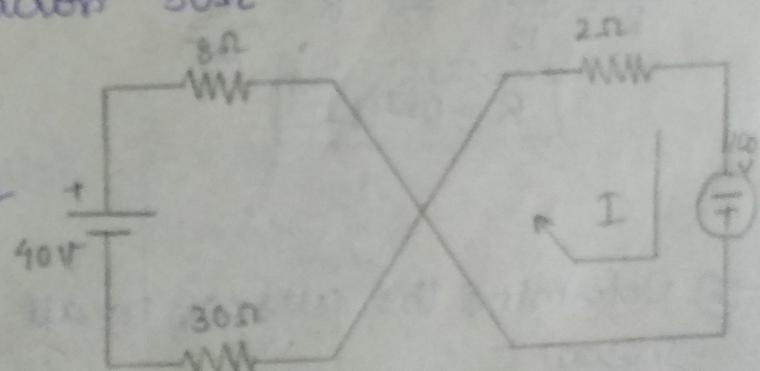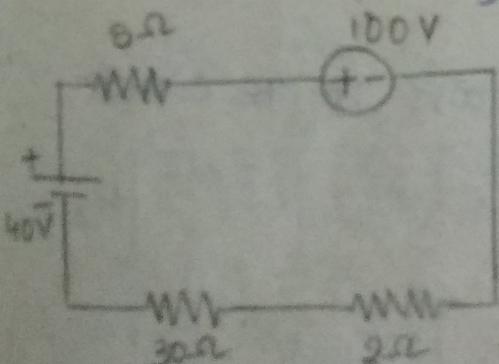

By redrawing the circuit we get I and V

$$(a) I = \frac{V_s}{R_{eq}}$$

$$R_{eq} = R_1 + R_2 + R_3$$

$$= 8 + 30 + 2$$

$$= 40\Omega$$

$$I = \frac{100 - 60}{40} = \frac{100 - 40}{40}$$

$$I = \frac{60}{40} = 1.5A$$

$$V_{30\Omega} = V_s \times \frac{\text{sum of } R}{\text{sum of } R}$$

$$= 40 \times \frac{30}{40} = 30V$$

⑤ Determine the parallel resistance between points A and B of the circuit shown in fig.

Sol: Given data

$$R_1 = 1\Omega \quad R_2 = 2\Omega \quad R_3 = 3\Omega$$

$$R_4 = 4\Omega$$


Req. of II<sup>nd</sup> connection

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$\frac{1}{R} = \frac{1}{1} + \frac{1}{2} + \frac{1}{3} + \frac{1}{4}$$

$$\frac{1}{R} = \frac{25}{12} \Rightarrow R = \frac{12}{25}$$

$$\boxed{R = 0.48\Omega}$$

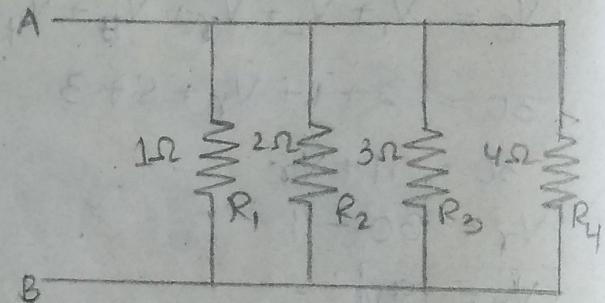


⑥ Determine the current in all resistors in the circuit shown.

Sol: Given data

$$I_f = 50A$$
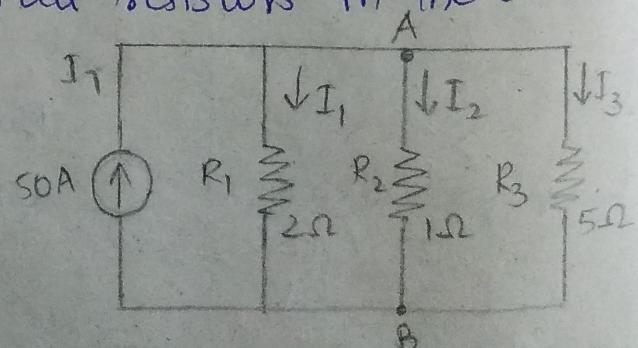
$$R_1 = 2\Omega, R_2 = 1\Omega, R_3 = 5\Omega$$



Req of 11<sup>th</sup> connection

$$\text{Req} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$\text{Req} = \frac{2 \times 1 \times 5}{2 \times 1 + 1 \times 5 + 5 \times 2} = 0.588 \Omega$$

By using current division rule,

$$I_1 = I_T \times \frac{\text{opposite } R}{\text{sum of } R}$$

$$= I_T \times \frac{R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} = 50 \times \frac{1 \times 5}{2 \times 1 + 1 \times 5 + 5 \times 2}$$

$$I_1 = 14.705 A$$

$$I_2 = I_T \times \frac{\text{opposite } R}{\text{sum of } R}$$

$$= I_T \times \frac{R_3 R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1} = 50 \times \frac{5 \times 2}{2 \times 1 + 1 \times 5 + 5 \times 2}$$

$$I_2 = 29.411 A$$

$$I_3 = I_T \times \frac{R_1 R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1} = 50 \times \frac{2 \times 1}{2 \times 1 + 1 \times 5 + 5 \times 2}$$

$$I_3 = 5.882 A$$

$$I_T = I_1 + I_2 + I_3$$


$$50A \approx 49.998 A$$


④ calculate the R equivalent between A and B terminals.

Sol:- 10Ω & 10Ω are in parallel

$$\text{Req} = \frac{R_1 R_2}{R_1 + R_2}$$

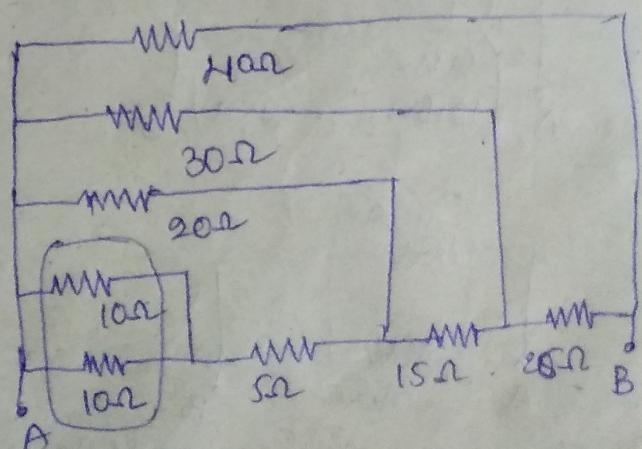
$$\text{Req} = \frac{10 \times 10}{10 + 10} = \frac{100}{20} = 5 \Omega$$



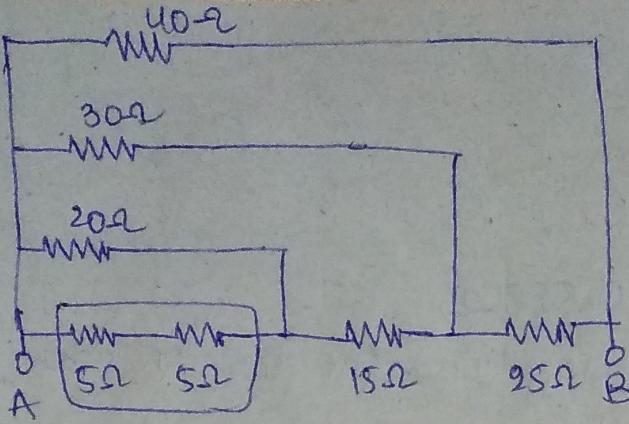


$5\Omega$  &  $5\Omega$  are in Series
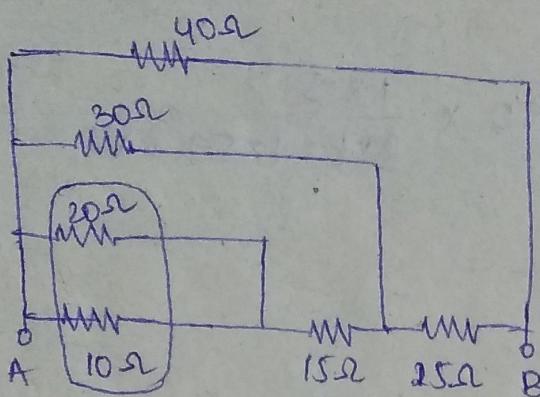
$$\begin{aligned} \text{Req} &= R_1 + R_2 \\ &= 5 + 5 = 10\Omega \end{aligned}$$




$10\Omega$  &  $20\Omega$  are in parallel
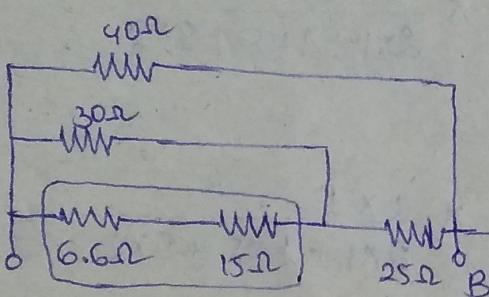
$$\begin{aligned} \text{Req} &= \frac{10 \times 20}{10 + 20} \\ &= 6.6\Omega \end{aligned}$$




$6.6\Omega$  &  $15\Omega$  are in series
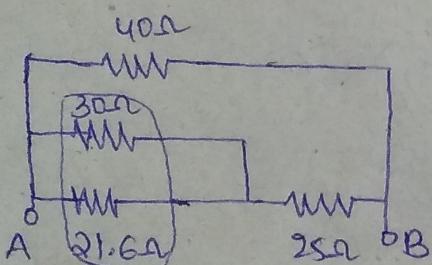
$$\begin{aligned} \text{Req} &= 6.6 + 15 \\ &= 21.6\Omega \end{aligned}$$




$30\Omega$  &  $21.6\Omega$  are in parallel
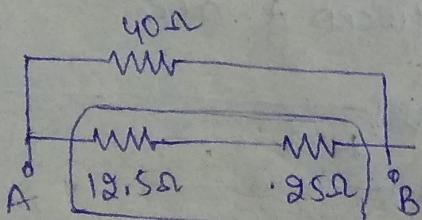
$$\text{Req} = \frac{30 \times 21.6}{30 + 21.6} = 12.5\Omega$$




$12.5\Omega$  &  $25\Omega$  are in series

$$\text{Req} = 12.5 + 25 = 31.5\Omega$$

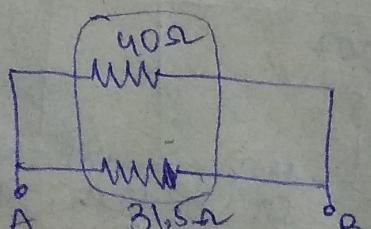



$31.5\Omega$  &  $40\Omega$  are in parallel
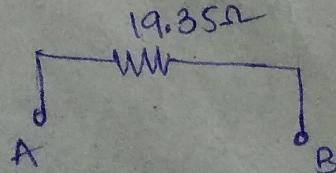
$$\begin{aligned} \text{Req} &= \frac{40 \times 31.5}{40 + 31.5} \\ &= 19.35\Omega \end{aligned}$$



Q) calculate the Equivalent between A and B terminals

Sol:-

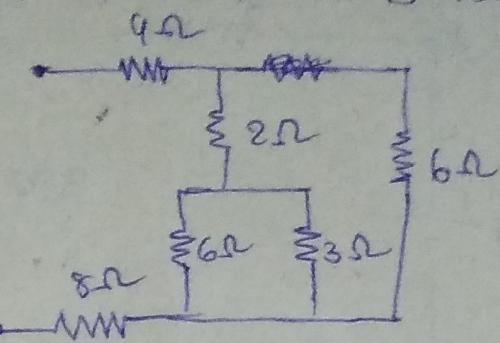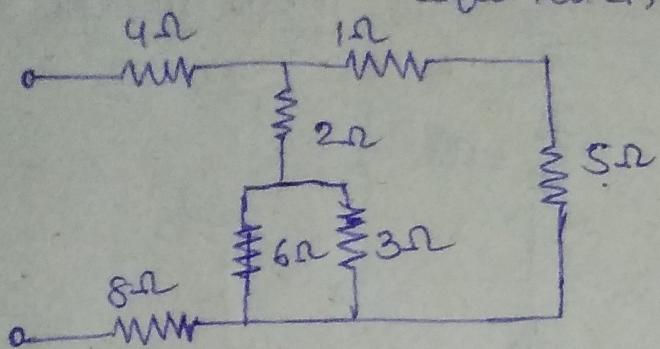


1Ω & 5Ω are in series

$$R_{eq} = 1 + 5 = 6\Omega$$


6Ω & 3Ω are in parallel
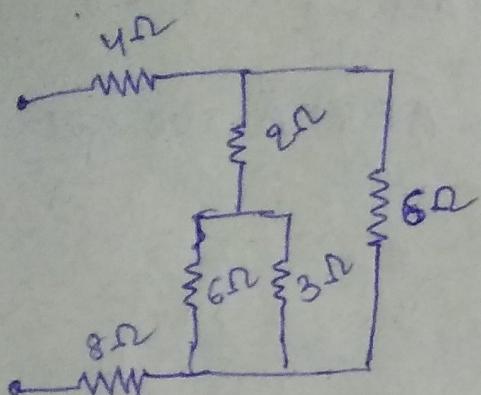
$$R_{eq} = \frac{3 \times 6}{3+6} = \frac{18}{9} = 2\Omega$$




2Ω & 2Ω are in series

$$R_{eq} = 2 + 2 = 4\Omega$$

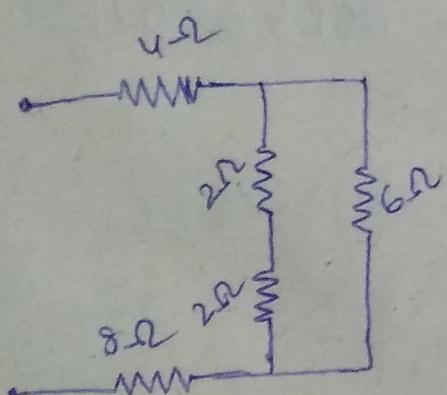


4Ω & 6Ω are in parallel

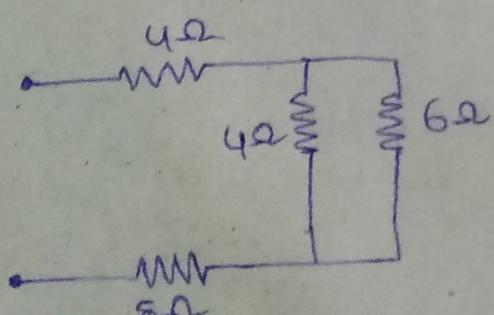
$$R_{eq} = \frac{4 \times 6}{4+6} = \frac{24}{10} = 2.4\Omega$$



4Ω & 2.4 & 8Ω are in series
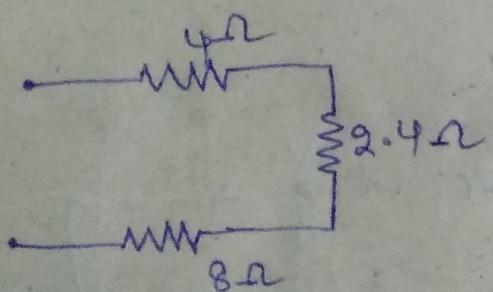
$$R_{eq} = 4 + 2.4 + 8 = \underline{\underline{14.4\Omega}}$$



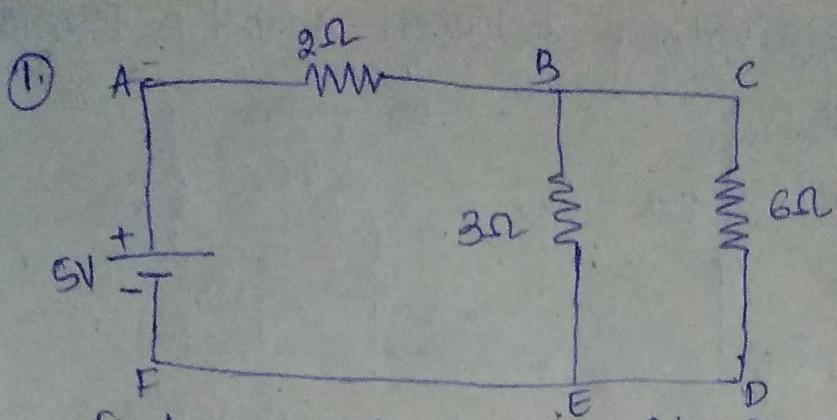

### Mesh Analysis

$$\text{find } I_{3\Omega} = ?$$

No. of meshes = 2

By applying KVL to 1<sup>st</sup> mesh i.e., ABEFA, we get

$$\Rightarrow 5V = 2I_1 + 3(I_1 - I_2)$$

$$5V = 2I_1 + 3I_1 - 3I_2$$

$$5V = 5I_1 - 3I_2 \quad \text{--- (1)}$$

By applying KVL to 2<sup>nd</sup> mesh i.e., BCDEB, we get

$$\Rightarrow 0 = 6I_2 + 3(I_2 - I_1)$$

$$= 6I_2 + 3I_2 - 3I_1$$

$$= 9I_2 - 3I_1 \quad \text{--- (2)}$$

By solving eqn ① & ②, we get

$$I_1 = 1.25A$$

$$I_2 = 0.4166A$$

$$I_{3\Omega} = I_1 - I_2 = 0.834A$$

(OR)

$$I_2 - I_1 = -0.834A$$

$V = 7.2$

Nodal Analysis  $I = \frac{V}{R}$

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_1 - 5}{2} + \frac{V_1}{3} + \frac{V_1}{6} = 0$$


$$\frac{3(V_1 - 5) + 2V_1 + V_1}{6} = 0$$


$$6V_1 - 15 = 0$$

$$V_1 = 15/6$$

$V_1 = 2.5$
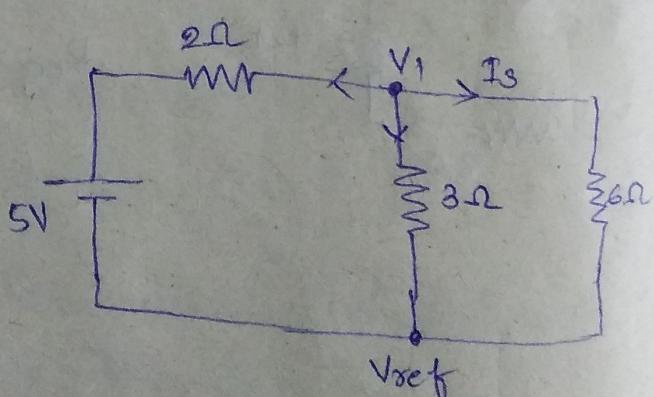
$$I_{3\Omega} = \frac{V_1 - 0}{3} = \frac{2.5}{3} = 0.83A$$



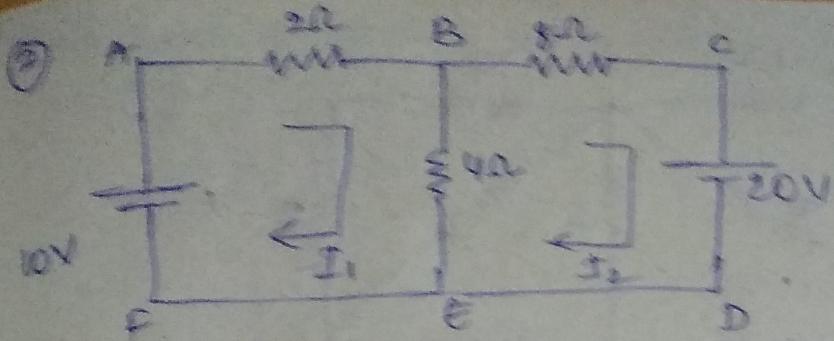

find  $I_{2\Omega} = ?$

By applying KVL to 1<sup>st</sup> mesh

$$\Rightarrow 10V = 2I_1 + 4(I_1 - I_2)$$

$$10V = 6I_1 - 4I_2 \quad \text{--- (1)}$$

By applying KVL to 2<sup>nd</sup> mesh

$$\Rightarrow 20V = 6(I_2 - I_1) + 8I_2$$

$$= 12I_2 - 4I_1$$

$$-20V = -4I_1 + 12I_2 \quad \text{--- (2)}$$

By solving (1) & (2), we get

$$I_1 = 0.714A$$

$$I_2 = -1.428A$$

$$\boxed{I_{2\Omega} = 0.714A = I_1}$$

Nodal

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_1 - 10}{2} + \frac{V_1}{4} + \frac{V_1 - 20}{8} = 0$$

$$\frac{4(V_1 - 10) + 2V_1 + V_1 - 20}{8} = 0$$


$$4V_1 - 40 + 2V_1 + V_1 - 20 = 0$$


$$7V_1 - 60 = 0$$

$$V_1 = \frac{60}{7}$$

$$V_1 = 8.57$$

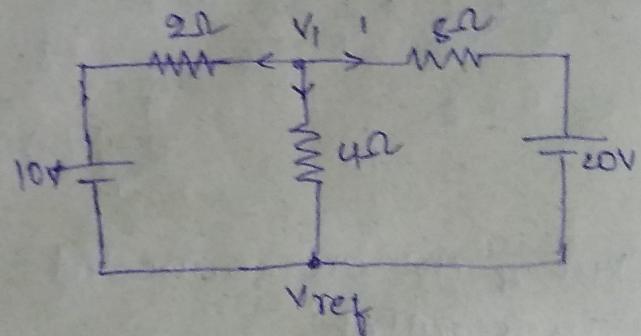
$$I_{2\Omega} = \frac{V_1 - 10}{2} = \frac{8.57 - 10}{2} = -0.174A \quad (\text{it is in opp. direction})$$



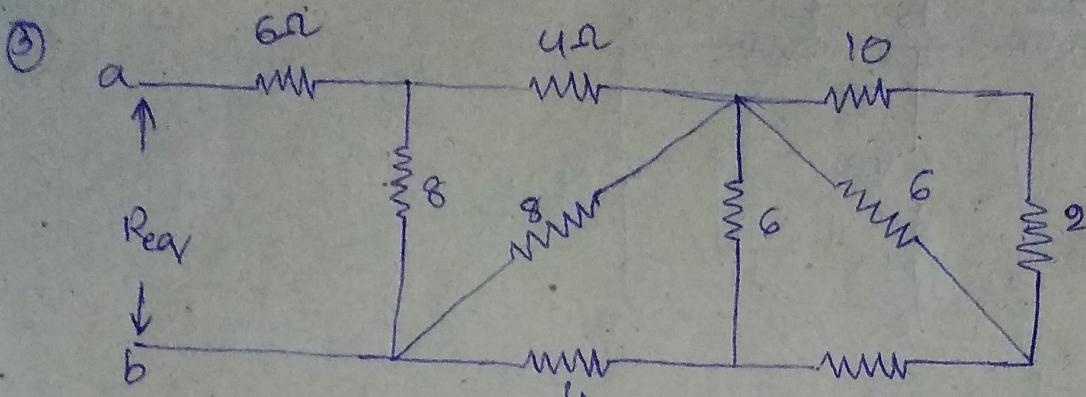

$10\Omega$  and  $2\Omega$  are connected in series
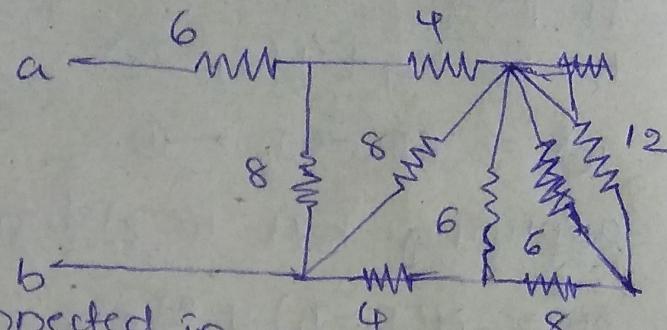
$$\begin{aligned} R_{eq} &= R_1 + R_2 \\ &= 10 + 2 \\ &= 12 \end{aligned}$$




~~$8\Omega$  and  $6\Omega$  are connected in parallel~~

$$\frac{1}{R} = \frac{1}{12} + \frac{1}{6}$$

$$= \frac{1}{4}$$

$$\boxed{R_{eq} = 4\Omega}$$

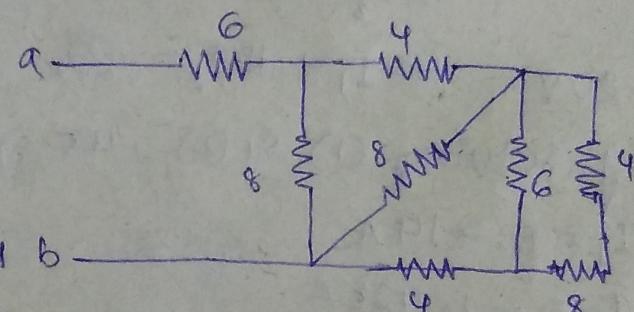

$6\Omega$  and  $8\Omega$  are connected in series

~~$\frac{1}{R} = \frac{1}{6} + \frac{1}{8} = \frac{5}{12}$~~


$$R_{eq} = 6 + 8$$

$$R = 14\Omega$$

$$\boxed{R_{eq} = 14\Omega}$$


$14\Omega$  &  $4\Omega$  are connected in parallel
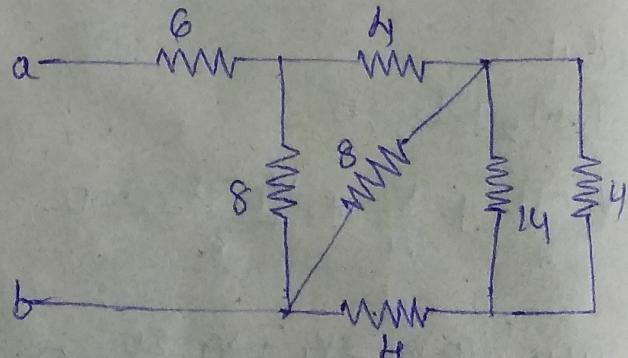
$$R_{eq} = \frac{14 \times 4}{14 + 4} = 3.11\Omega$$




$4\Omega$  &  $3.11\Omega$  are in series

$$4 + 3.11 = 7.11\Omega$$

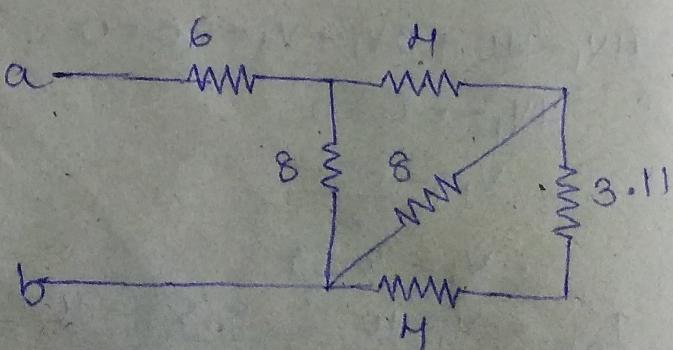


$8\Omega$  and  $7.11\Omega$  are connected in parallel.
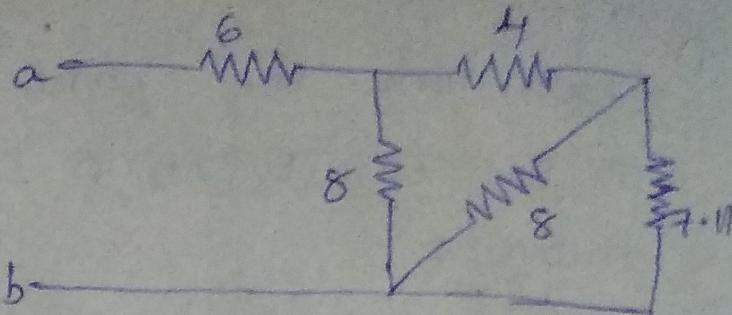
$$R_{eq} = \frac{8 \times 7.11}{8 + 7.11}$$
$$= 3.764\Omega$$



$8\Omega$  and  $3.764\Omega$  are in parallel

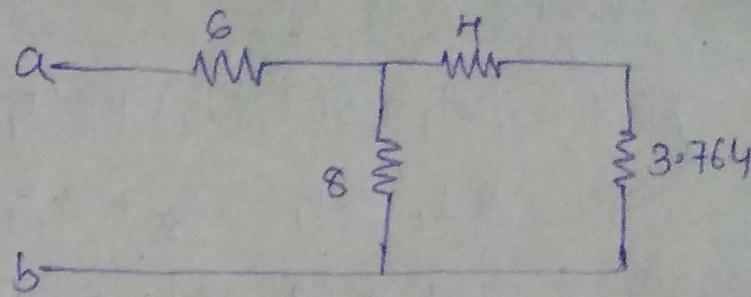
$$R_{eq} = \frac{8 \times 3.764}{8 + 3.764}$$
$$= 2.559\Omega$$



$12\Omega$ ,  $6\Omega$  &  $2.559\Omega$  are connected in series

$$R_{eq} = R_1 + R_2 + R_3$$
$$= 6 + 4 + 2.559$$
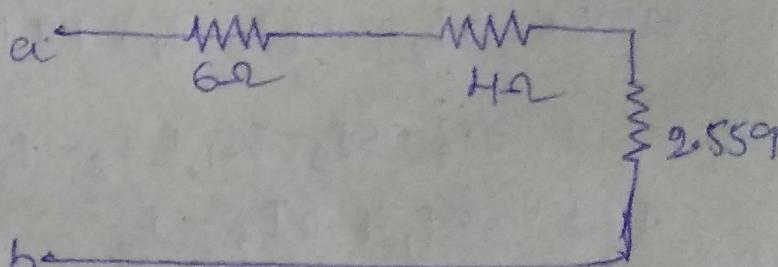
$$R_{eq} = \underline{\underline{12.559\Omega}}$$



27/5/22 HUO


- ① Determine the power absorbed by  $5\Omega$  resistor in the circuit shown below by using mesh analysis:

Ans: By applying KVL to 1st mesh i.e., ABCFA, we get

$$50V = 10I_1 + 5(I_1 - I_2) + 3(I_1 - I_3)$$

$$50 = 10I_1 + 5I_1 - 5I_2 + 3I_1 - 3I_3$$
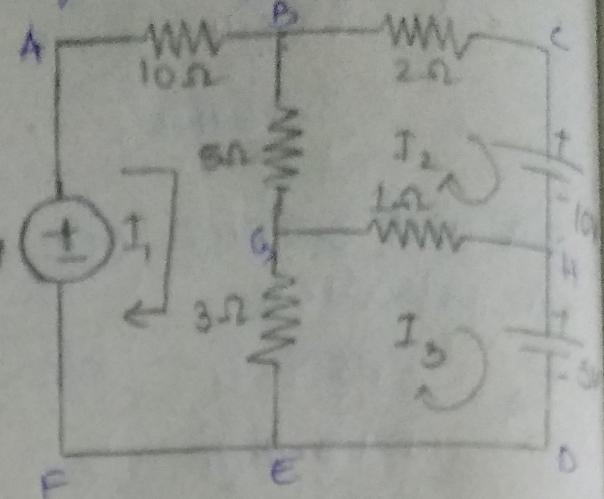
$$50 = 18I_1 + 5I_2 - 3I_3 \quad \text{--- (1)}$$



By applying KVL to 2nd mesh i.e., BCHGB, we get

$$-10V = 2I_2 + 5(I_2 - I_1) + 1(I_2 - I_3)$$

$$= 2I_2 + 5I_2 - 5I_1 + I_2 - I_3$$

$$-10 = -5I_1 + 8I_2 - I_3 \quad \text{--- (2)}$$

By applying KVL to 3rd mesh i.e., GHDEG, we get

$$-5 = 3(I_3 - I_1) + 1(I_3 - I_2)$$

$$-5 = 3I_3 - 3I_1 + I_3 - I_2$$

$$-5 = -3I_1 - I_2 + 4I_3 \quad \text{--- (3)}$$

By solving eqn's (1), (2) & (3), we get

$$\begin{aligned} I_1 &= \frac{1175}{356} & I_2 &= \frac{355}{356} & I_3 &= \frac{525}{356} \\ &= 3.3006A & &= 0.99719A & &= 1.4747A \end{aligned}$$

$$P_{5\Omega} = ? \quad [P = V \times I \quad (\because V = IR)]$$

$$P = \Sigma R \times I$$

$$I_{5\Omega} = I_1 - I_2 \text{ or } I_2 - I_1$$

$$= 3.30341 \quad = -2.30341A \text{ (opp direction)}$$

$$\begin{aligned} P_{5\Omega} &= I^2 R \\ &= 26.52W \end{aligned}$$

22/5/22

(10) Solve the circuit by mesh analysis and find current in all branches.

Sol:- By applying KVL to 1<sup>st</sup> mesh ABGHA, we get

$$125V = 5I_1 + 3(I_1 - I_2)$$

$$125 = 5I_1 + 3I_1 - 3I_2$$

$$125 = 8I_1 - 3I_2 \quad \dots \textcircled{1}$$

By applying KVL to 2<sup>nd</sup> mesh BCFGD, we get

$$0 = 3(I_2 - I_1) + 2I_2 + 4(I_2 - I_3)$$

$$= 3I_2 - 3I_1 + 2I_2 + 4I_2 - 4I_3$$

$$0 = -3I_1 + 9I_2 - 4I_3 \quad \dots \textcircled{2}$$

By applying KVL to 3<sup>rd</sup> mesh CDEFB, we get

$$-300 = 4(I_3 - I_2) + 6I_3$$

$$-300 = 4I_3 - 4I_2 + 6I_3$$

$$-300 = 10I_3 - 4I_2 \quad \dots \textcircled{3}$$

Solving eqn's  $\textcircled{1}$ ,  $\textcircled{2}$  &  $\textcircled{3}$ , we get

$$I_1 = 11.254 A = I_{5\Omega}$$

$$I_2 = -11.653 A = I_{2\Omega}$$

$$I_3 = -34.661 A = I_{6\Omega}$$

$$I_{3\Omega} = I_1 - I_2 = 22.907 A$$


(or)

$$I_2 - I_1 = -22.907 A$$


$$I_{4\Omega} = I_2 - I_3 = 23.008 A$$

(or)

$$I_3 - I_2 = -23.008 A$$

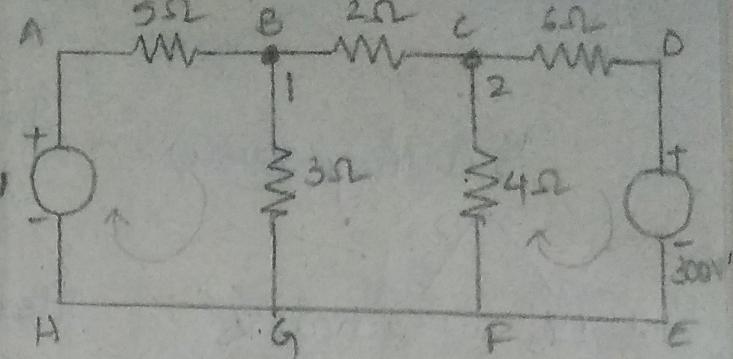


## Types of Sources

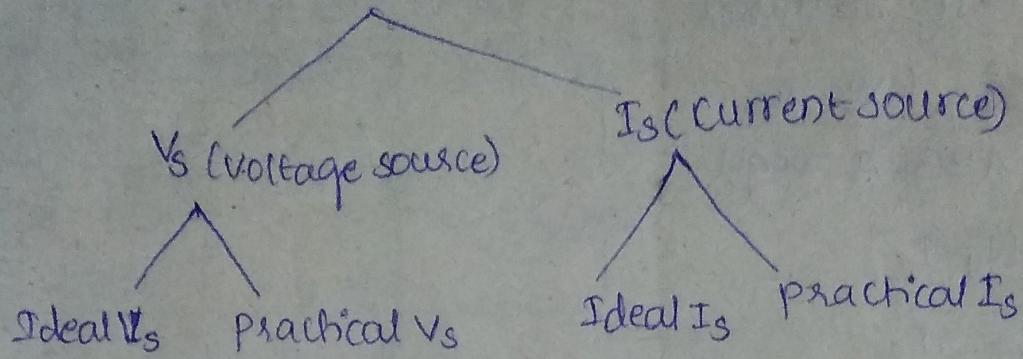

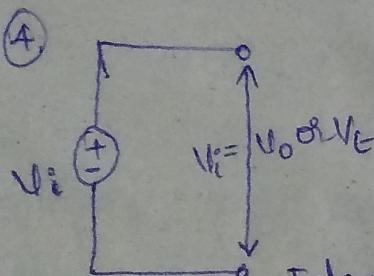
### Ideal sources

- ① Ideal sources are imaginary sources.
- ② There is no internal resistance.
- ③ The voltage drop is zero.  
 $(R=0)$




Ideal voltage source

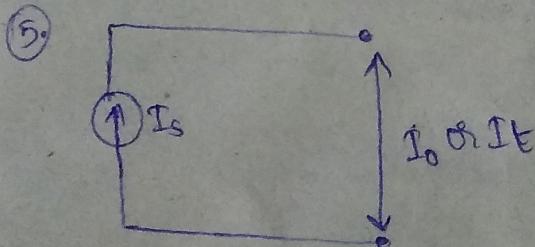


Ideal current source

- ⑥ V-I characteristics of ideal sources

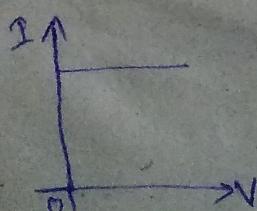

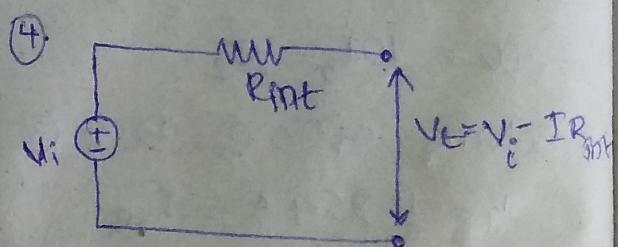
### Practical sources


- ① Ideal Practical sources are real sources.
- ② There is a internal resistance.
- ③ Voltage drop occurs



Practical voltage source

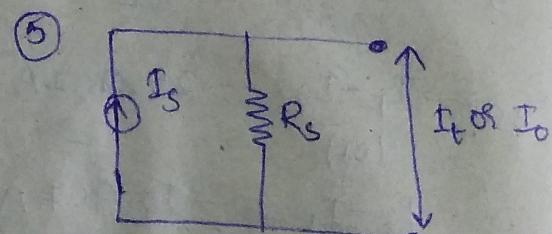

Practical current source

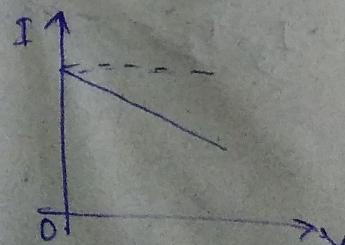

7. It provides constant values of current and voltages

8. It is not applicable for the circuits.

9. It gives only theoretical values

7. It provides variable values of current and voltages.

8. It is applicable

9. It gives both practical & theoretical values.

### Classification of sources

#### Dependent sources


- i) VCVs
- ii) NCCS
- iii) CCVs
- iv) CCCS

#### Independent sources


- i) Vs
- ii) Is

### Dependent Sources:

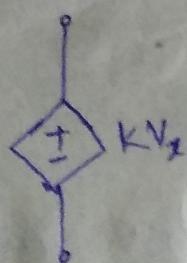(i) Voltage control Voltage source (VCVs):  
This source produces voltage as a function of voltage. S1




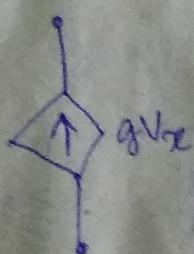(ii) Voltage control current source (VCCS):  
This source produces voltage as a function of current.



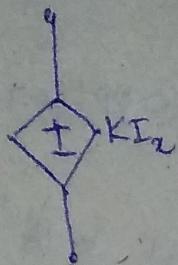
### (iii) Current Control Voltage Source: (CCVS)

This source produces current as the function of voltage.



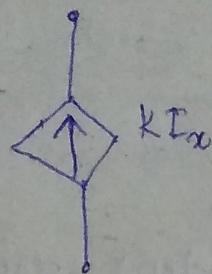
### (iv) Current control current source: (CCCS)

This source produces current as the function of current.



### Independent Sources:

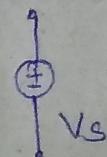


#### (i) Independent Voltage source:


The source which produces voltages without depending upon the other circuit parameters (or) components.
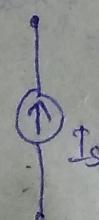
#### (ii) Independent current source:

The source which produces current without depending upon the other circuit parameters (or) components.



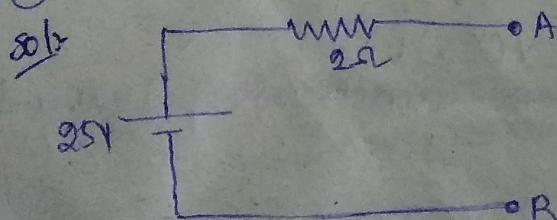
#### ① Find the equivalent current source




$$I_s = ?$$

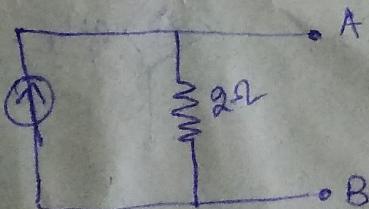
$$I_s = \frac{V_s}{R_s} = \frac{25}{2} = 12.5 \text{ A}$$



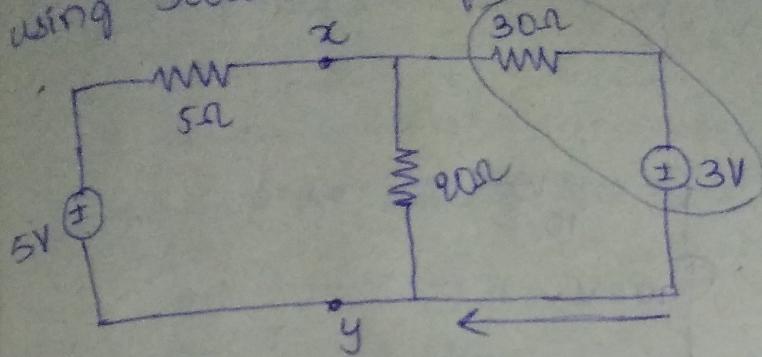Determine current by reducing the circuit to the right side of xy terminals to its simplest form by using source transformation technique.




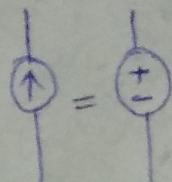
$$I_S = \frac{V_S}{R} = \frac{3}{30} = 0.1A$$




$20\Omega$  &  $30\Omega$  are in parallel,

$$R_{eq} = \frac{20 \times 30}{20 + 30} = \frac{20 \times 30}{50}$$

$$R_{eq} = 12\Omega$$

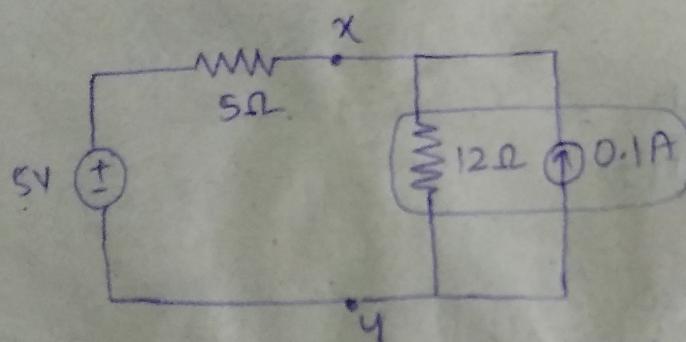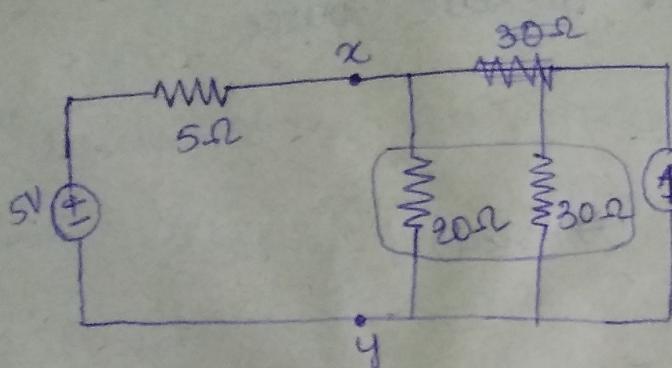

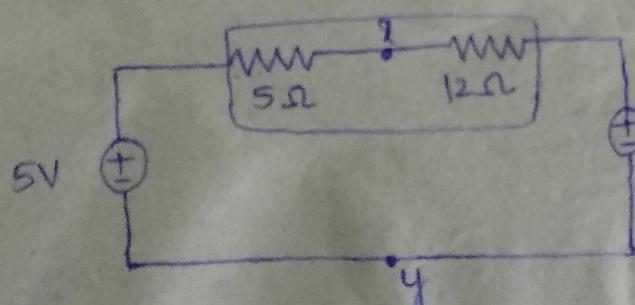
$$V_S = I \times R = 0.1 \times 12 = 1.2V$$




$5\Omega$  &  $12\Omega$  are in series,

$$R_{eq} = 5 + 12 = 17\Omega$$

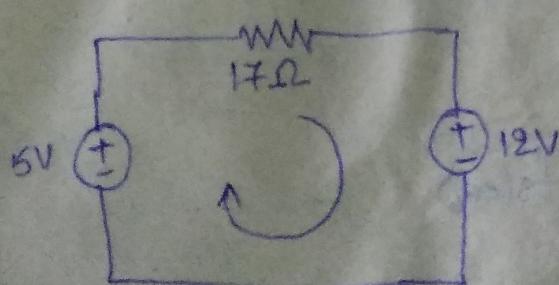

By applying KVL, we get

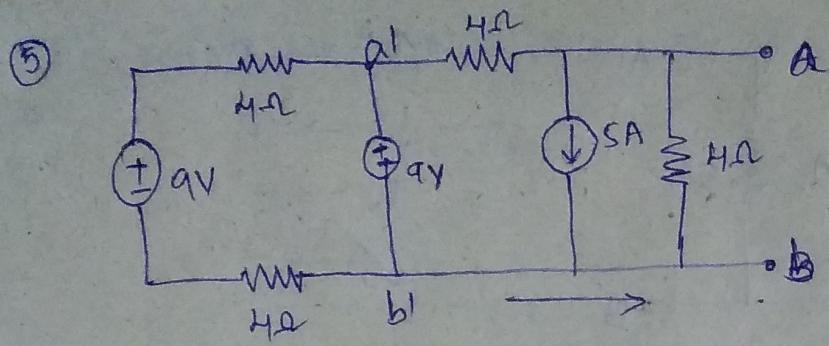
$$\begin{aligned} V_S &= V_1 \\ \Rightarrow 5 + I_1 &= 17 \\ \Rightarrow I_1 &= \underline{\underline{0.235A}} \end{aligned}$$



$$\Rightarrow I_S = \frac{V_S}{R} = \frac{9}{4} = 2.25A$$


Use source transformation to convert the current circuit (i.e. a'b') to a single current source.

Converting  $V_S$  into  $I_S$

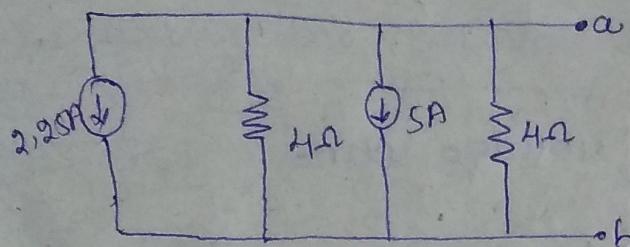


since both the currents are in same direction we can add them.
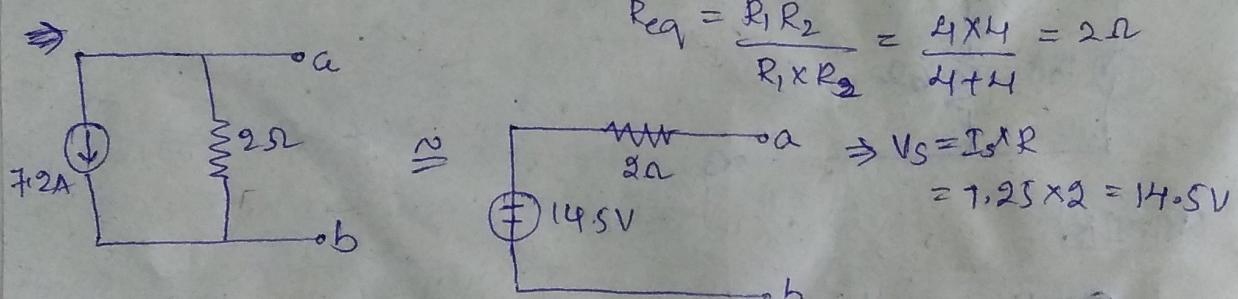
$$\Rightarrow I_T = 2.25 + 5 = 7.25A ; 4\Omega \text{ & } 4\Omega \text{ are in parallel,}$$



Converting the current source into voltage source.

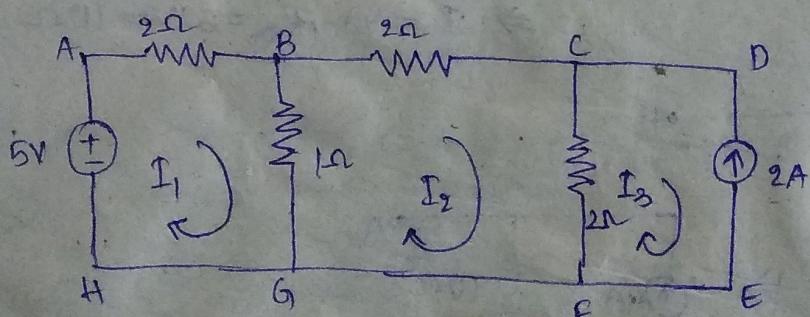⑥ Determine the current in all branches by mesh analysis and nodal analysis.



Mesh :-

By applying KVL to 1st mesh ABGHA, we get

$$5 = 2I_1 + 1(I_1 - I_2)$$

$$5 = 3I_1 - I_2 \rightarrow ①$$

By applying KVL to III mesh BCFG, we get

$$0 = 2I_2 + 2(I_2 - I_3) + 1(I_2 - I_1)$$

$$0 = -I_1 + 5I_2 - 2I_3 \rightarrow ②$$

By from III mesh,  $I_3 = -2A$

$$\text{sub } I_3 = -2A \text{ in } ② \Rightarrow -4 = -I_1 + 5I_2 \rightarrow ③$$

sol ① & ③

$$I_{2a} \text{ or } I_1 = 1.5A$$

$$I_{2a} \text{ or } I_2 = -0.5A$$

(II mesh)



$$I_{1a} = I_1 - I_2 \text{ or } I_2 - I_1 \\ = 2A$$

$$I_{2a} = I_2 - I_3 \text{ or } I_3 - I_2$$

$$= 1.5A$$

II method: By transforming the current source we get the following circuit
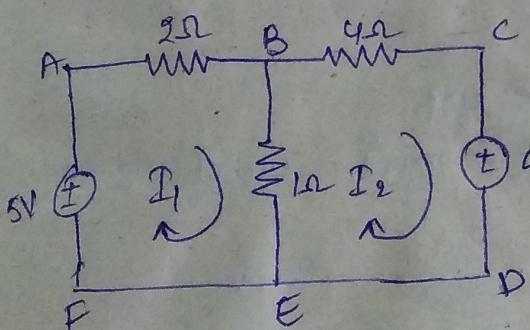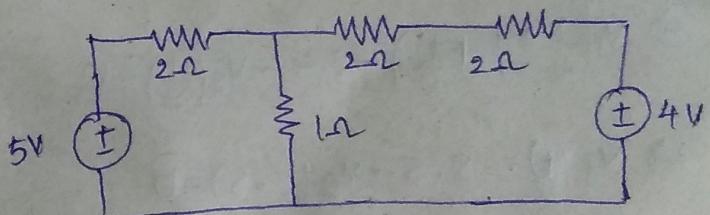
$$V_s = I_s \times R \\ = 2 \times 2 \\ = 4V$$



By applying KVL to I mesh ABFEA, we get

$$5 = 2I_1 + 1(I_1 - I_2)$$

$$5 = 3I_1 - I_2 \rightarrow ①$$

By applying KVL to II mesh BCDEB, we get

$$-4 = 1(I_2 - I_1) + 4I_2$$


$$-4 = -I_1 + 5I_2 \rightarrow ②$$

$$\text{By solving } ① \text{ & } ② \cdot I_1 = 1.5A \quad I_2 = -0.5A$$

or  
 $I_{2a}$  or  
 $I_{4a}$

$$I_{1a} = I_1 - I_2 \text{ or } I_2 - I_1 \\ = 2A$$

Nodal analysis:

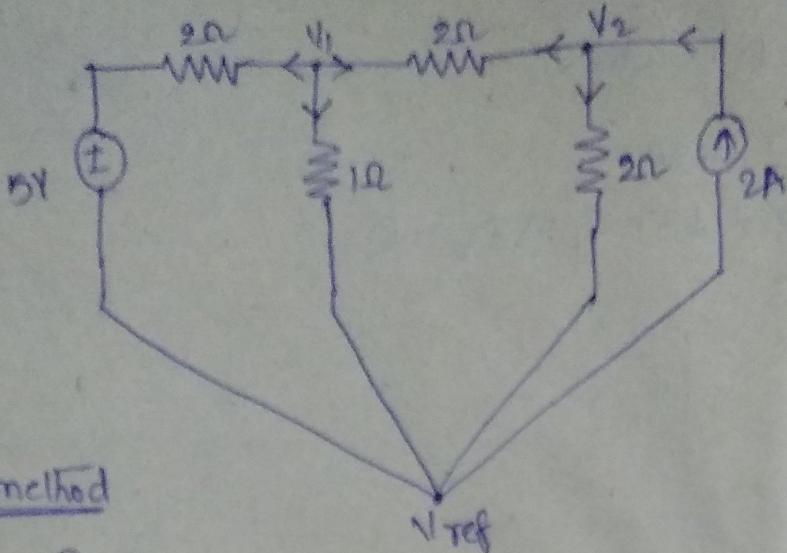

I method

$$I = \frac{V}{R}$$

By applying KCL to node 1, we get

$$\frac{V_1 - 5}{2} + \frac{V_1}{1} + \frac{V_1 - V_2}{2} = 0$$

$$\Rightarrow \frac{V_1}{2} + \frac{V_1}{1} + \frac{V_1}{2} - \frac{5}{2} - \frac{V_2}{2} = 0$$

$$\Rightarrow V_1 \left( \frac{1}{2} + \frac{1}{1} + \frac{1}{2} \right) - 2.5 - V_2 \left( \frac{1}{2} \right) = 0$$

$$\Rightarrow V_1 (2) - 2.5 - V_2 (0.5) = 0$$

$$2V_1 - V_2 (0.5) = 2.5 \quad \text{--- (1)}$$

By applying KCL to node 2, we get

$$\frac{V_2 - V_1}{2} + \frac{V_2}{2} - 2 = 0$$

sum of Incoming I = sum of outgoing I

$$\frac{V_2}{2} - \frac{V_1}{2} + \frac{V_2}{2} = 2$$

$$V_2 \left( \frac{1}{2} + \frac{1}{2} \right) - V_1 \left( \frac{1}{2} \right) = 2$$

$$-0.5V_1 + V_2 = 2 \rightarrow \text{--- (2)}$$

By solving (1) & (2), we get  $V_1 = 2V$

$$I_{2A} (\text{at node 1}) = \frac{V_1 - 5}{2} = \frac{2 - 5}{2} = -1.5A$$


$$V_2 = 3V$$

$$I_{2A} = \frac{V_2}{1} = 2A$$

$$I_{2A} (\text{combination branch}) = \frac{V_1 - V_2}{2} \text{ or } \frac{V_2 - V_1}{2} = \frac{2 - 3}{2} = -\frac{1}{2} = -0.5A$$

$$I_{2\Omega} (\text{at node 2}) = \frac{V_2}{2} = \frac{3}{2} = 1.5A$$

I method:

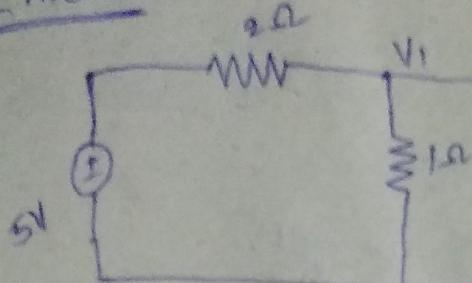

By S-T of the I.s into V.s  
⇒  $V_S = I_S \times R = 2 \times 2 = 4V$

$$\Rightarrow V_S = 4V$$

$$\Rightarrow V_S = I_S \times R = 2 \times 2 = 4V$$

By applying KCL at node 1, we get

$$\frac{V_1 - 5}{2} + \frac{V_1}{1} + \frac{V_1 - 4}{4} = 0$$

$$\Rightarrow \frac{V_1}{2} - \frac{5}{2} + \frac{V_1}{1} + \frac{V_1}{4} - \frac{4}{4} = 0 \Rightarrow V_1 \left( \frac{1}{2} + \frac{5}{2} + \frac{1}{4} \right) - \frac{5}{2} - \frac{4}{4} = 0$$




$$\Rightarrow V_1 (1.75) = 3.5 \Rightarrow V_1 = 2V$$

$$I_{2\Omega} = \frac{V_1 - 5}{2} = \frac{2 - 5}{2} = -\frac{3}{2} = -1.5A$$

$$I_{1\Omega} = \frac{V_1}{1} = 2A$$

$$I_{4\Omega} = \frac{V_1 - 4}{4} = \frac{2 - 4}{4} = -\frac{2}{4} = -0.5A$$

② Find out the voltages at the nodes

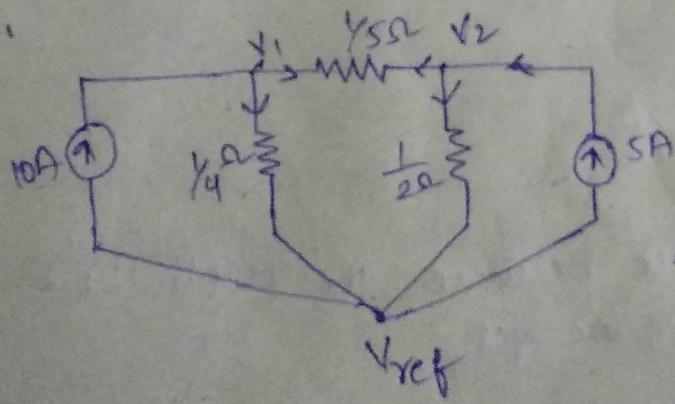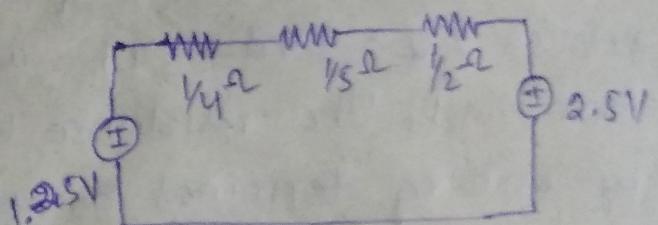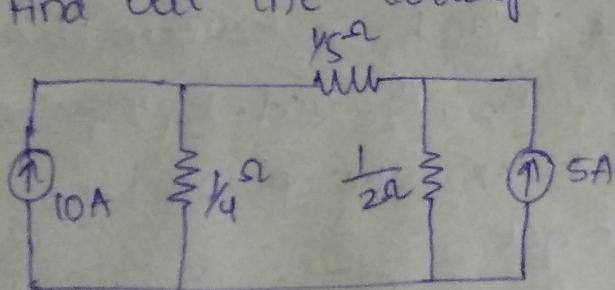

By applying KCL to node 1  
we get  
 $\sum \text{e.i} = \sum \text{l.i}$

$$\Rightarrow 10 = \frac{V_1}{1/4} + \frac{V_1 - V_2}{1/2}$$

$$10 = 4V_1 + 5V_1 - 5V_2$$

$$10 = 9V_1 - 5V_2 \quad \text{--- (1)}$$

By applying KCL to node 2, we get  
 sum of e.i.r = sum of l.s

$$5 = \frac{V_2 - V_1}{R_5} + \frac{V_2}{R_2}$$


$$5 = 5V_2 - 5V_1 + 2V_2$$

$$5 = 7V_2 - 5V_1 \quad \text{By solving } ① \text{ & } ②, \text{ we get}$$


$$V_1 = 2.5 \text{ V}$$

$$V_2 = 2.5 \text{ V}$$

### Derivation of Delta to Star:

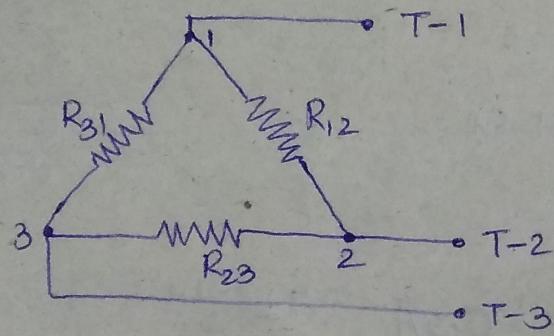

fig(1)

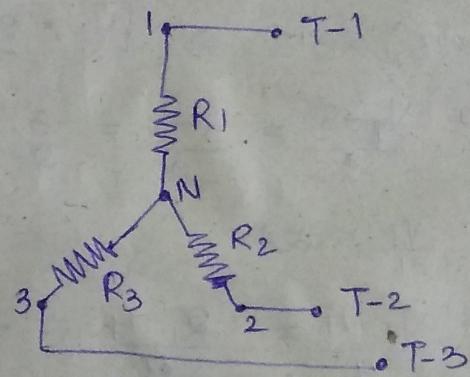

fig(2)

Consider a delta system with three corner points 1, 2 & 3 across three terminals as shown in figure.

Electrical resistance of the branch is between 1 & 2 points, 2 & 3 and 3 & 1 are  $R_{12}$ ,  $R_{23}$  and  $R_{31}$  respectively from fig 1. The resistance between the points 1 & 2 by ignoring terminal -3, we get

$$(R_{23} + R_{31}) \parallel R_{12}$$

$$\frac{R_{12}(R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \rightarrow ①$$

from fig(2), The resistance between the points 1 & 2 by ignoring terminal -3, we get

$$R_1 + R_2 \rightarrow ②$$

Equating eq<sup>n</sup> ① & ② [∴ Two systems are identical,  
 If R measured b/w 1 & 2 will be same]

$$\Rightarrow R_1 + R_2 = \frac{R_{12}(R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \rightarrow ③$$

similarly, by ignoring terminal 2, we get

$$\Rightarrow R_1 + R_3 = \frac{R_{31}(R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} \rightarrow ④$$

By ignoring terminal -1, we get

$$R_2 + R_3 = \frac{R_{23}(R_{12} + R_{31})}{R_{12} + R_{23} + R_{31}} \rightarrow ⑤$$

NOW, we subtract eq<sup>n</sup> ⑤ from eq<sup>n</sup> ③

$$R_1 - R_3 = R_{12}R_{23} + R_{12}$$

$$(R_1 + R_2) - (R_2 + R_3) = \frac{R_{12}(R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} - \frac{R_{23}(R_{12} + R_{31})}{R_{12} + R_{23} + R_{31}}$$

$$R_1 - R_3 = \frac{R_{12}R_{23} + R_{12}R_{31} - R_{23}R_{12} - R_{23}R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_1 - R_3 = \frac{R_{12}R_{31} - R_{23}R_{31}}{R_{12} + R_{23} + R_{31}} \rightarrow ⑥$$

Adding eq<sup>n</sup> ④ & eq<sup>n</sup> ⑥

$$(R_1 + R_3) + (R_1 - R_3) = \frac{R_3(R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} + \frac{R_{12}R_{31} - R_{23}R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$2R_1 = \frac{R_{12}R_{31} + R_{23}R_{31} + R_{12}R_{31} - R_{23}R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$2R_1 = \frac{2(R_{12}R_{31})}{R_{12} + R_{23} + R_{31}}$$


$$R_1 = \frac{R_{12}R_{31}}{R_{12} + R_{23} + R_{31}} \rightarrow ⑦$$

Similarly, we get  $R_2$  &  $R_3$  by using another combination  
 of subtraction & addition with eq<sup>n</sup> ③, ④, ⑤


$$R_2 = \frac{R_{23}R_{12}}{R_{12} + R_{23} + R_{31}} \rightarrow ⑧$$

$$R_3 = \frac{R_{23}R_{31}}{R_{12} + R_{23} + R_{31}} \rightarrow ⑨$$

## Derivation of star to Delta:

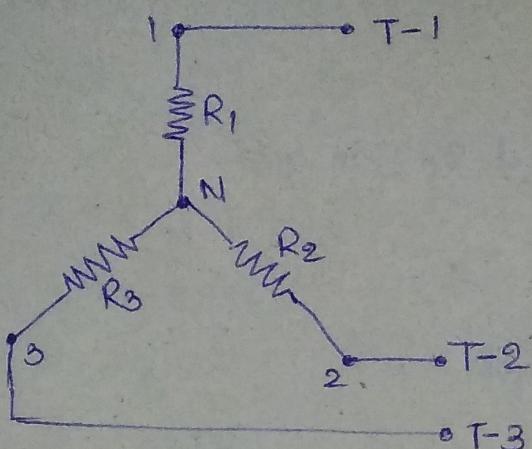

fig(1)

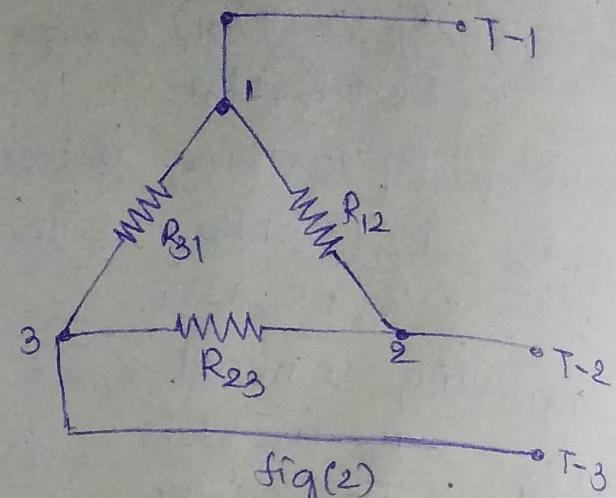

fig(2)

Consider three resistances  $R_1, R_2$ , &  $R_3$  connected in star as shown in fig(1)

In order to get the equivalent Delta of the given star, we take the help of Delta-star transformation eqns ⑦, ⑧ & ⑨

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}} \rightarrow ⑦$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}} \rightarrow ⑧$$

$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}} \rightarrow ⑨$$

Now by multiplying  $⑦ \times ⑧$ ,  $⑧ \times ⑨$  &  $⑨ \times ⑦$  we get

$$⑦ \times ⑧ \Rightarrow R_1 R_2 = \frac{R_{12}^2 R_{23} R_{31}}{(R_{12} + R_{23} + R_{31})^2} \rightarrow ⑩$$

$$⑧ \times ⑨ \Rightarrow R_2 R_3 = \frac{R_{12} R_{23}^2 R_{31}}{(R_{12} + R_{23} + R_{31})^2} \rightarrow ⑪$$

$$⑨ \times ⑦ \Rightarrow R_3 R_1 = \frac{R_{12} R_{23} R_{31}^2}{(R_{12} + R_{23} + R_{31})^2} \rightarrow ⑫$$

Now, Add ⑩, ⑪ & ⑫ eqns

$$\Rightarrow R_1 R_2 + R_2 R_3 + R_3 R_1 =$$

$$= \frac{R_{12}^2 R_{23} R_{31}}{(R_{12} + R_{23} + R_{31})^2} + \frac{R_{12} R_{23}^2 R_{31}}{(R_{12} + R_{23} + R_{31})^2} + \frac{R_{12} R_{23} R_{31}^2}{(R_{12} + R_{23} + R_{31})^2}$$

$$= \frac{R_{12} R_{23} R_{31}}{(R_{12} + R_{23} + R_{31})} (R_{12} + R_{23} + R_{31})$$

$$\Rightarrow R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{12} R_{23} R_{31}}{(R_{12} + R_{23} + R_{31})}$$

sub  $\boxed{\frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}} = R_1$  by eqn ⑦

$$\Rightarrow R_1 R_2 + R_2 R_3 + R_3 R_1 = R_1 R_{23}$$

$$\Rightarrow R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$\Rightarrow R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1} \rightarrow ⑬$$

similarly, by substituting remaining values, we can write relations for  $R_{12}$  &  $R_{31}$

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3} \rightarrow ⑭$$

$$\text{and } R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2} \rightarrow ⑮$$

$D \rightarrow S$

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$$


$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$S \rightarrow D$


$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$
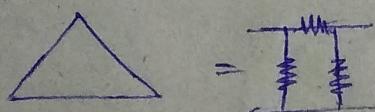
$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$




Delta is also represented as  $\Pi$

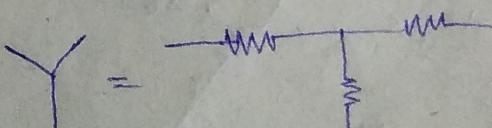

star is also represented as T-shape

① Transform the given circuit into star.

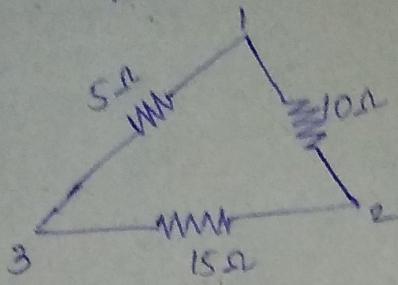

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_1 = \frac{10 \times 5}{10 + 15 + 5}$$


$$R_1 = 1.66\Omega$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$$


$$R_2 = \frac{10 \times 15}{10 + 15 + 5} \Rightarrow R_2 = 5\Omega$$

$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$
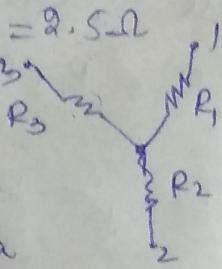
$$R_3 = \frac{15 \times 5}{10 + 15 + 5} = 2.5\Omega$$



② Transform the given diagram into Delta

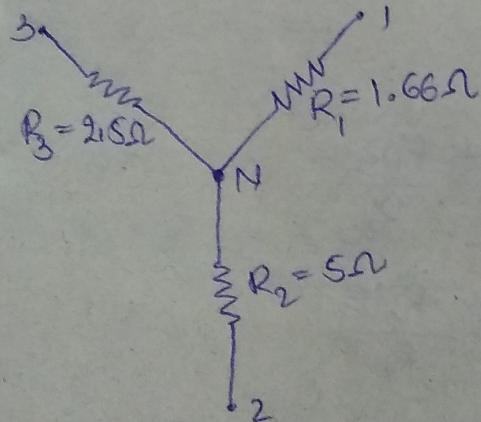

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{12} = 1.66 + 5 + \frac{1.66 \times 5}{2.5}$$

$$R_{12} = 9.98\Omega$$


$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_{23} = 15.03\Omega$$


$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$

$$R_{31} = 2.5 + 1.66 + \frac{2.5 \times 1.66}{5}$$

$$R_{31} = 4.99\Omega$$

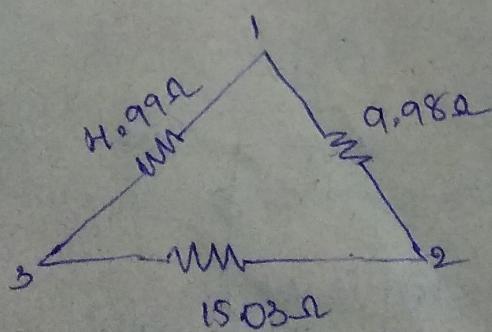

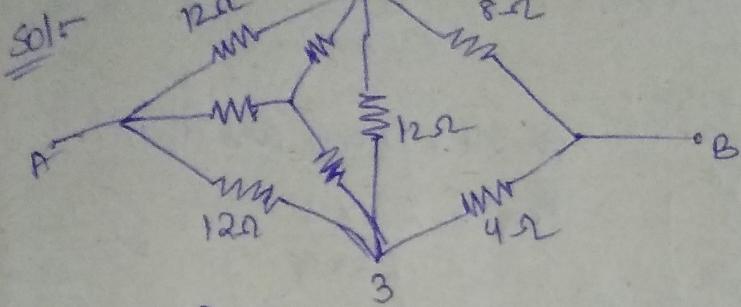③ calculate the Req using by Delta to star transformation



$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$


$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_1 = \frac{12 \times 12}{12 + 12 + 12}$$

$$R_2 = 4\Omega$$

$$R_3 = 4\Omega$$

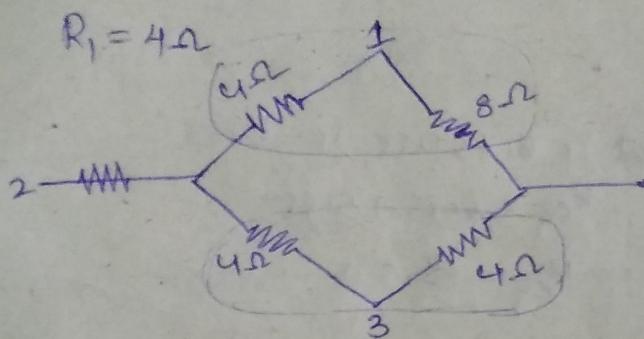


$4\Omega \& 8\Omega$  are in series,

$$Req = 4 + 8 = 12\Omega$$


$4\Omega \& 4\Omega$  are in series,

$$Req = 4 + 4 = 8\Omega$$

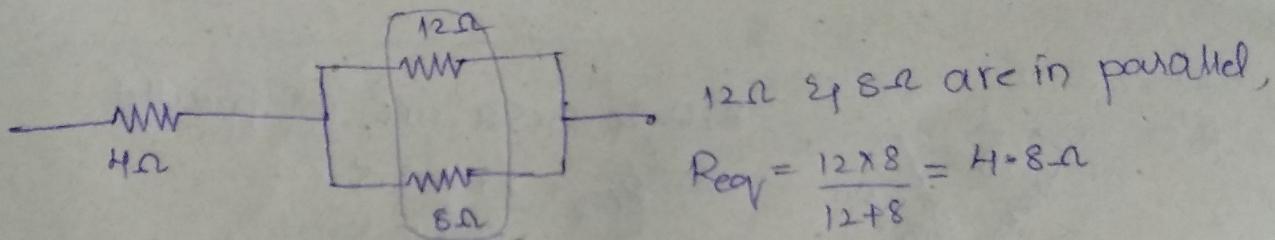


$12\Omega \& 8\Omega$  are in parallel,
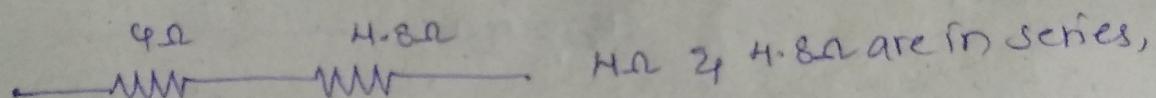
$$Req = \frac{12 \times 8}{12 + 8} = 4.8\Omega$$




$4\Omega \& 4.8\Omega$  are in series,

$$Req = 4 + 4.8 = 8.8\Omega$$

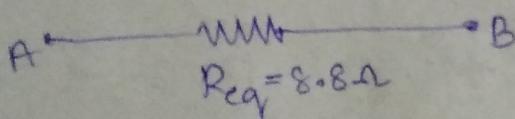

Calculate  
④ Req by Star to Delta.

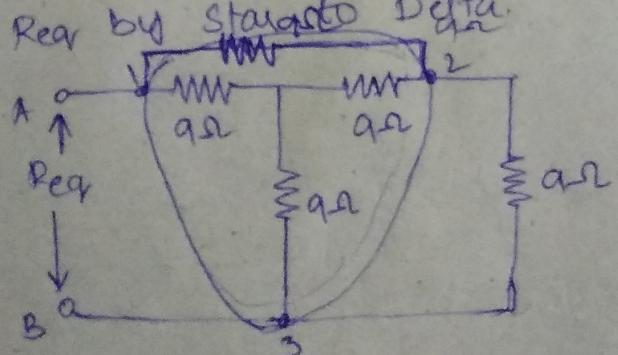

The Star  $\rightarrow$  D

$$R_{12} = R_1 + R_2 + \frac{R_1 \times R_2}{R_3}$$

$$R_{12} = 9 + 9 + \frac{9 \times 9}{9}$$


$$R_{12} = 27\Omega$$

$$R_{23} = R_1 + R_3 + \frac{R_2 \times R_3}{R_1}$$

$$R_{23} = 27\Omega$$

$$R_{31} = R_3 + R_1 + \frac{R_3 \times R_1}{R_2}$$

$$R_{31} = 27\Omega$$

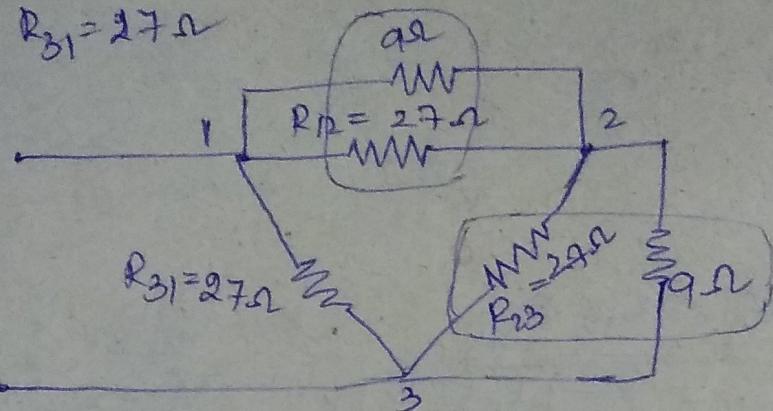


$\Rightarrow 27\Omega$  &  $9\Omega$  are in  $\parallel$

$$R_{eq} = \frac{27 \times 9}{27+9}$$

$$R_{eq} = 6.75\Omega$$

$\Rightarrow 27\Omega$  &  $9\Omega$  are in  $\parallel$  across II & III nodes,

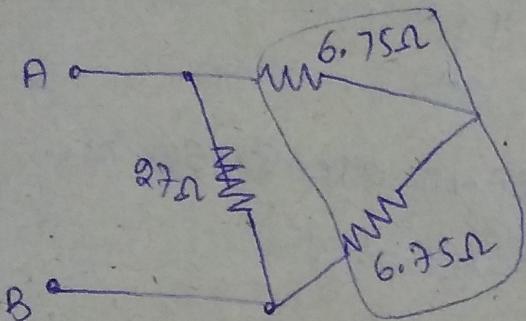
$$R_{eq} = \frac{27 \times 9}{27+9} = 6.75\Omega$$



$6.75\Omega$  &  $6.75\Omega$  are in series

$$R_{eq} = 6.75 + 6.75$$


$$R_{eq} = 13.5\Omega$$

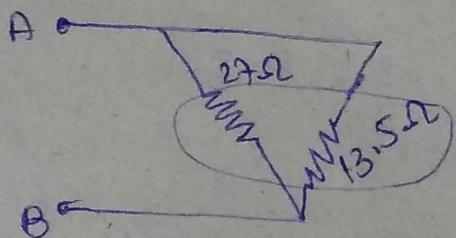

$27\Omega$  &  $13.5\Omega$  are in parallel


$$R_{eq} = \frac{27 \times 13.5}{27+13.5}$$

$$R_{eq} = 9\Omega$$

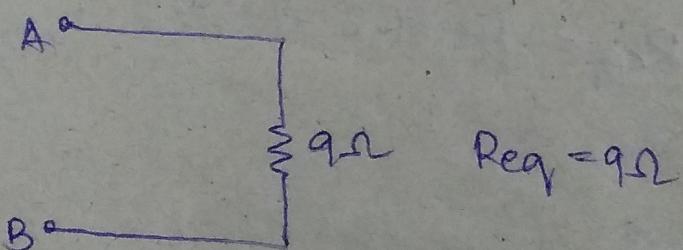


$$R_{eq} = 9\Omega$$

11/6/22

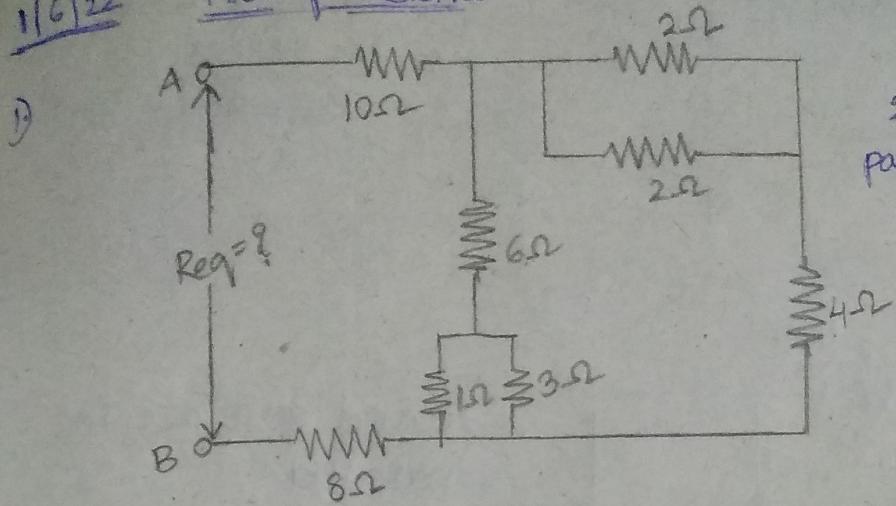Hw problems

$2\Omega$  &  $2\Omega$  are in parallel

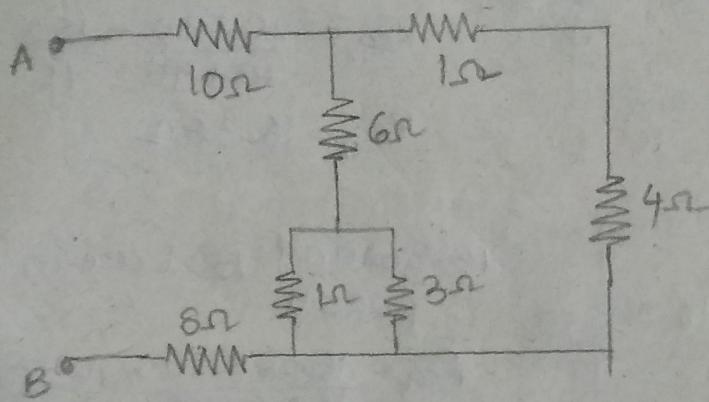
$$Req = \frac{2 \times 2}{2+2} = \frac{4}{4} = 1\Omega$$



$1\Omega$  and  $4\Omega$  are in series


$$Req = 1+4$$

$$Req = 5\Omega$$

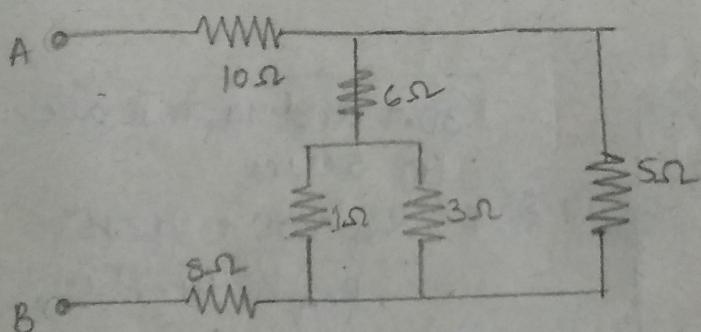


$1\Omega$  and  $3\Omega$  are in parallel
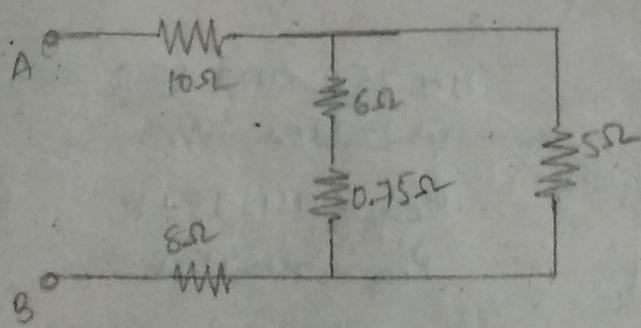
$$Req = \frac{1 \times 3}{1+3} = \frac{3}{4} = 0.75\Omega$$



$6\Omega$  and  $0.75$  are in series


$$6 + 0.75 = 6.75\Omega$$

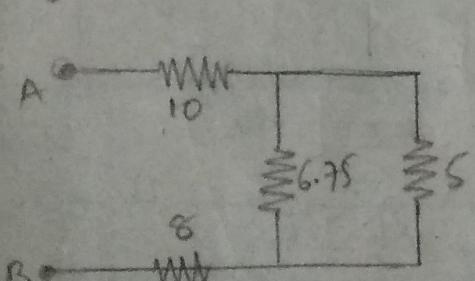

$6.75$  and  $5\Omega$  are in parallel

$$\frac{6.75 \times 5}{6.75+5} = 2.87$$







$$Req = \frac{20.87}{20.87}$$

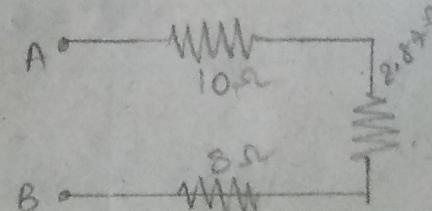

$10\Omega$ ,  $8\Omega$  &  $2.87$  are in series



$$Req = 10 + 8 + 2.87$$

$$Req = 20.87\Omega$$

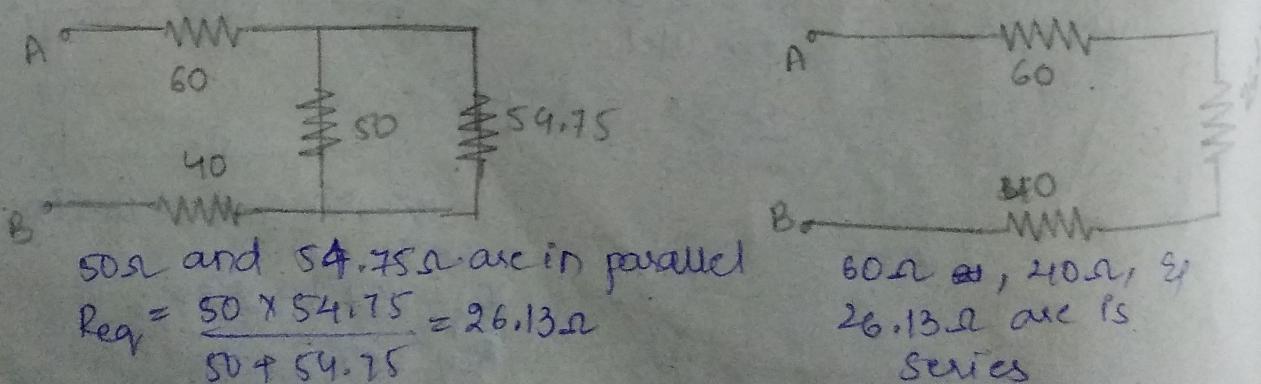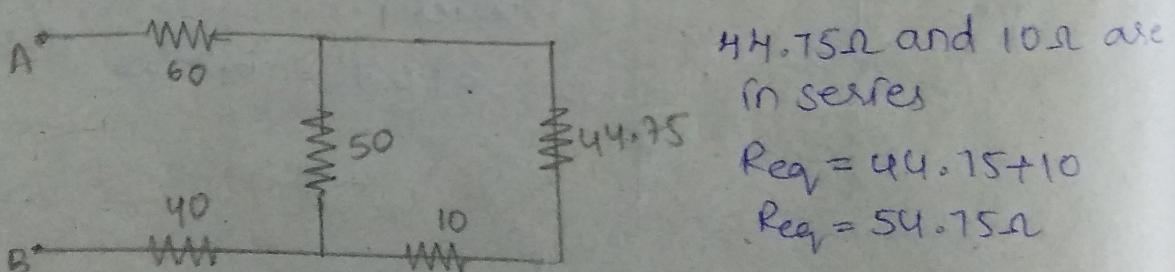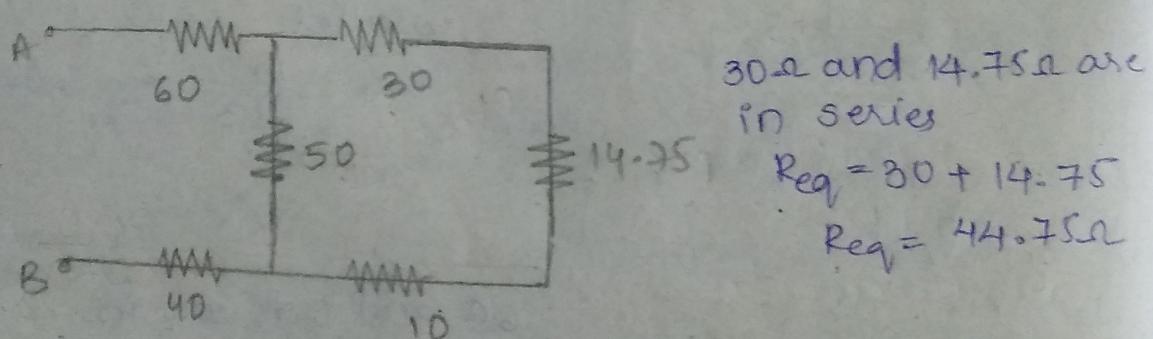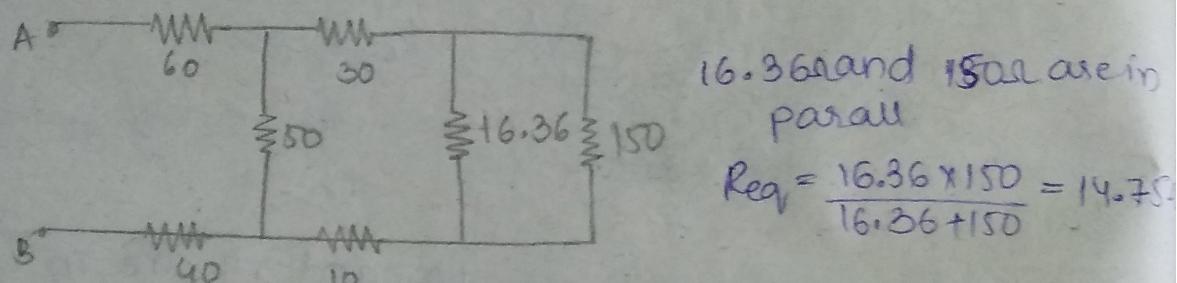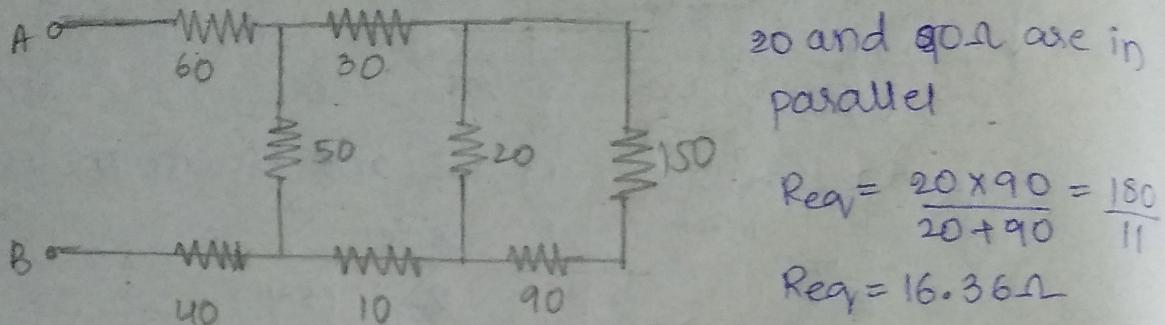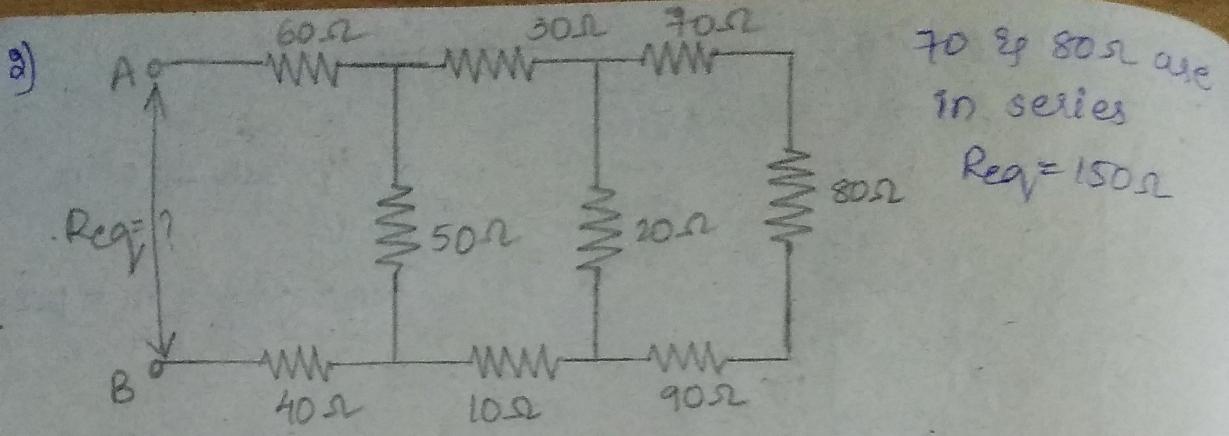

$$R_{eq} = 60 + 40 + 26.13$$

$$R_{eq} = \underline{126.13\Omega}$$

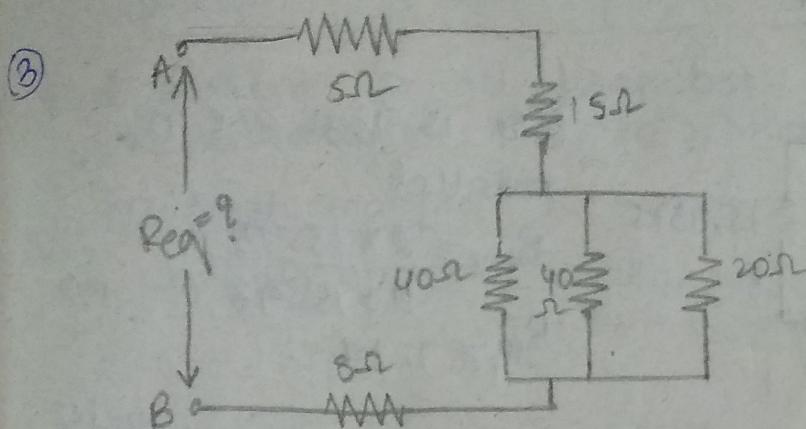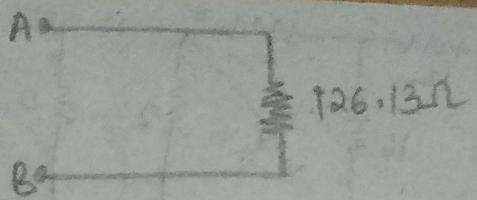


40, 40, 20Ω are in parallel

$$R_{eq} = \frac{1}{20} + \frac{1}{40} + \frac{1}{40}$$

$$\frac{1}{R} = \frac{1}{10}$$


$$R = 10\Omega$$

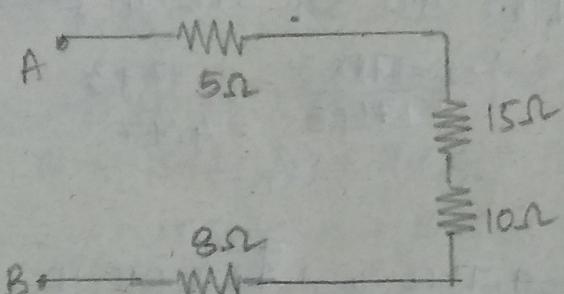

15Ω & 10Ω are in series

$$R_{eq} = 15 + 10$$



$$R_{eq} = 25\Omega$$

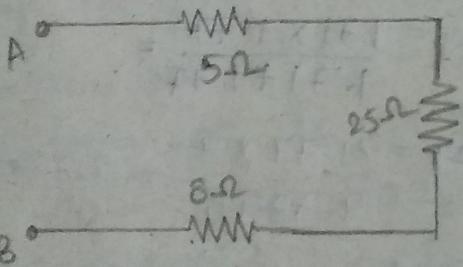

5Ω, 25Ω, 8Ω are in series

$$R_{eq} = 5 + 25 + 8$$


$$R_{eq} = \underline{38\Omega}$$

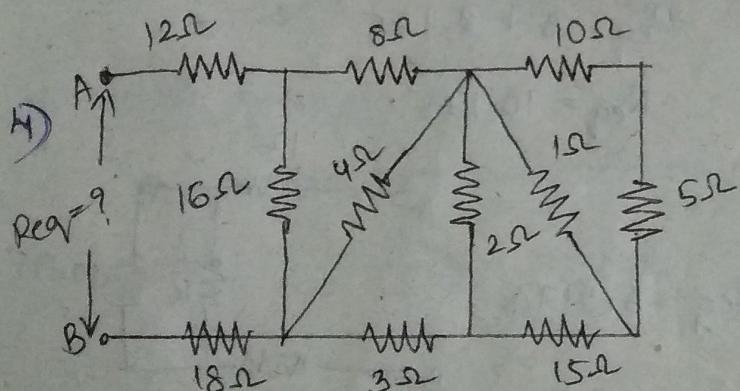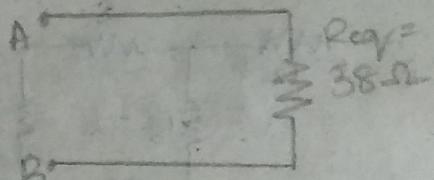

10Ω & 5Ω are in series

$$R_{eq} = 10 + 5$$


$$R_{eq} = 15\Omega$$

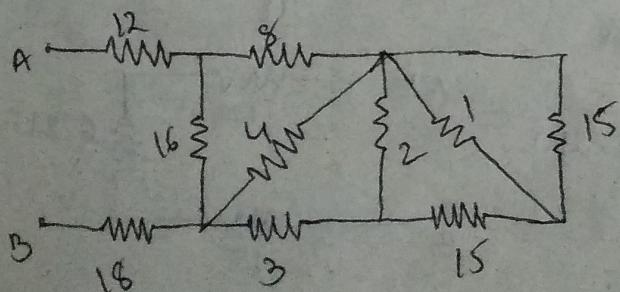


12Ω & 15Ω are in parallel

$$R_{eq} = \frac{1 \times 15}{1 + 15}$$

$$R_{eq} = \frac{15}{16} = 0.9375$$

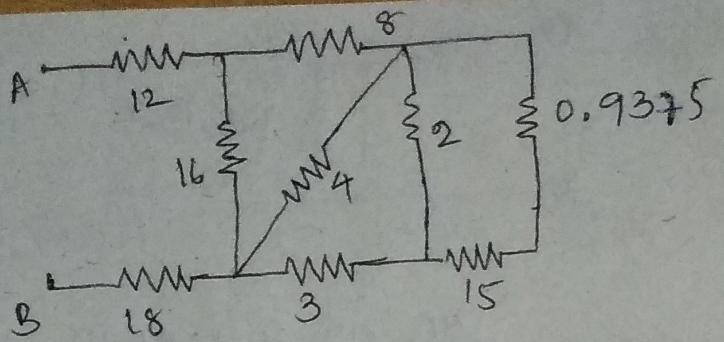

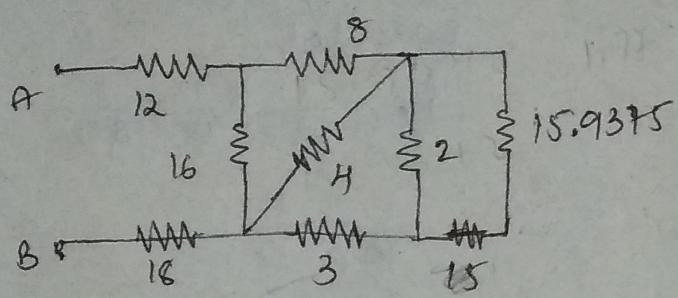
$15\Omega$  &  $0.9375\Omega$  are  
in series  
 $Req = 15 + 0.9375\Omega$



2 &  $15.93\Omega$  are in  
parallel


$$Req = \frac{2 \times 15.93}{2 + 15.93}$$

$$Req = 1.77$$

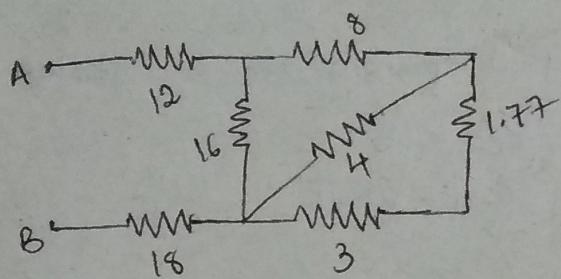

$1.77\Omega$  and  $3\Omega$  are in parallel

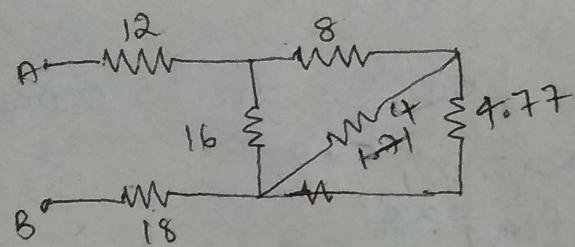
$$Req = \frac{1.77 \times 3}{1.77 + 3} = 1.77 + 3 = 4.77$$



$4.77\Omega$  &  $1.77\Omega$  are in  
parallel

$$Req = \frac{1.77 \times 4.77}{1.77 + 4.77} =$$
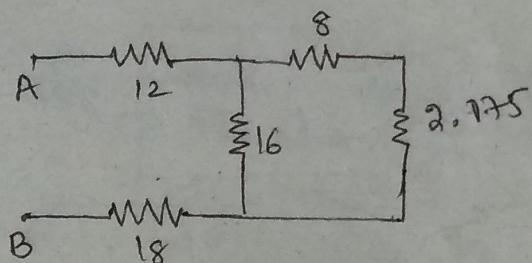
$$Req = \frac{4.77 \times 4}{4.77 + 4} = 2.175$$



$8\Omega$  and  $2.175\Omega$  are in  
series

$$Req = 8 + 2.175$$




$$Req = 10.175$$


$16\Omega$  &  $10.175\Omega$  are in  
parallel

$$Req = \frac{16 \times 10.175}{16 + 10.175} \Rightarrow Req = 6.219\Omega$$

$12\Omega$ ,  $6.21\Omega$  and  $18\Omega$  are in  
series
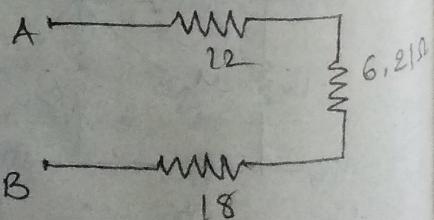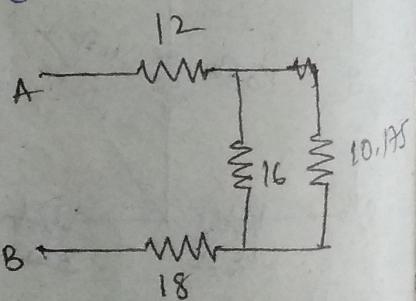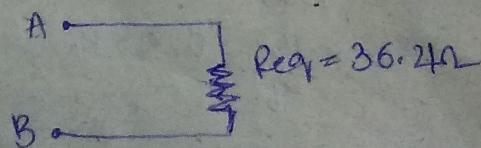
$$Req = 12 + 6.21 + 18 \Rightarrow Req = 36.21\Omega$$



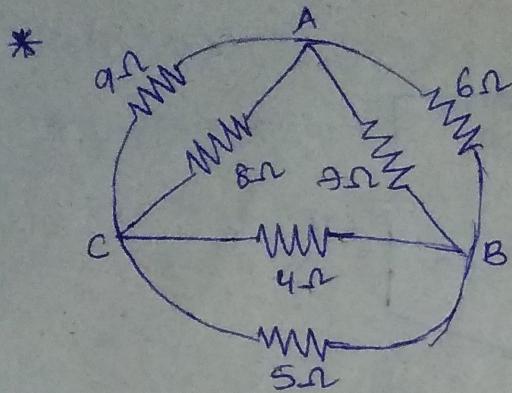

Determine the equivalent star.

9 ohm and 8 ohm are in parallel connection

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{9(8)}{9+8} = 4.23\Omega$$

6 ohm and 7 ohm are in parallel connection

$$R_{eq} = \frac{6(7)}{6+7} = 3.23\Omega$$

5 ohm and 4 ohm are in parallel connection

$$R_{eq} = \frac{4(5)}{4+5} = 2.22\Omega$$

converting Delta to star

$$R_{12} = 3.23\Omega, R_{23} = 2.22\Omega$$

$$R_{31} = 4.23\Omega$$

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$= \frac{3.23(4.23)}{3.23 + 2.22 + 4.23}$$



$$R_1 = 1.411\Omega$$


$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{3.23(2.22)}{3.23 + 2.22 + 4.23}$$

$$R_2 = 0.740\Omega$$

$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{2.22 \times 4.23}{3.23 + 2.22 + 4.23}$$

$$R_3 = 0.97\Omega$$

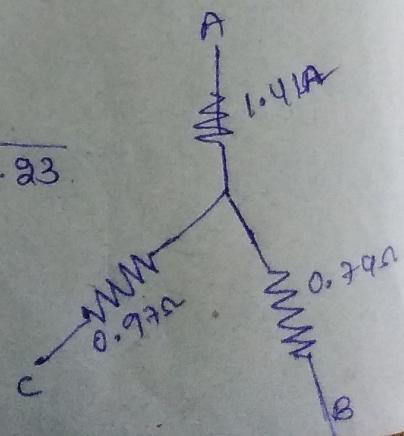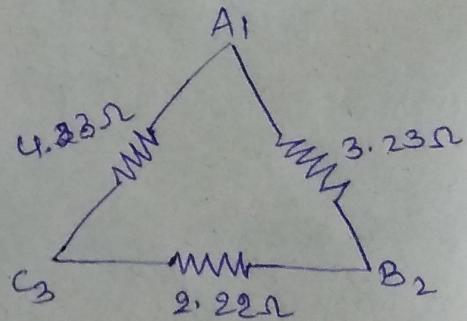

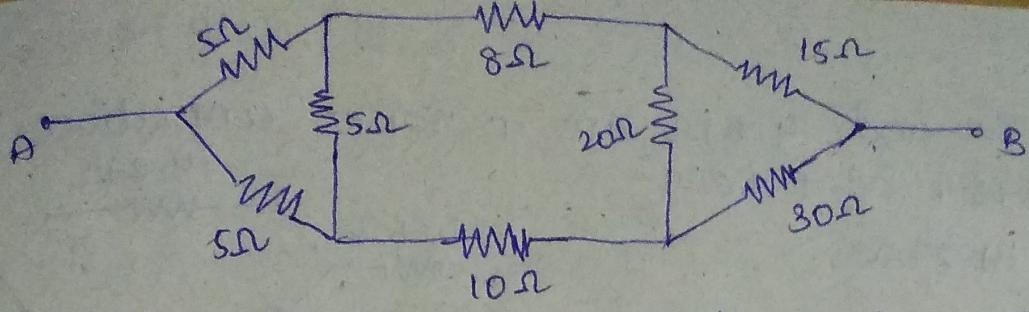

Calculate current when  $V=30$  by using star to Delta transformation.


Converting from Delta to Star

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_1 = \frac{5(s)}{5+s+5} = \frac{25}{15} = 1.66\Omega$$

$$R_{23} = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{5(s)}{5+s+5} = 1.66\Omega$$
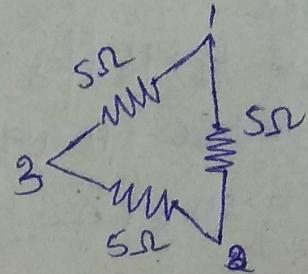
$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{5(s)}{5+s+5} = 1.66\Omega$$






For II<sup>nd</sup> Delta

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{15(20)}{15+30+20} = 4.61\Omega$$


$$R_2 = \frac{R_{23} R_{12}}{R_{12} + R_{23} + R_{31}} = \frac{30(15)}{15+30+20} = 6.92\Omega$$
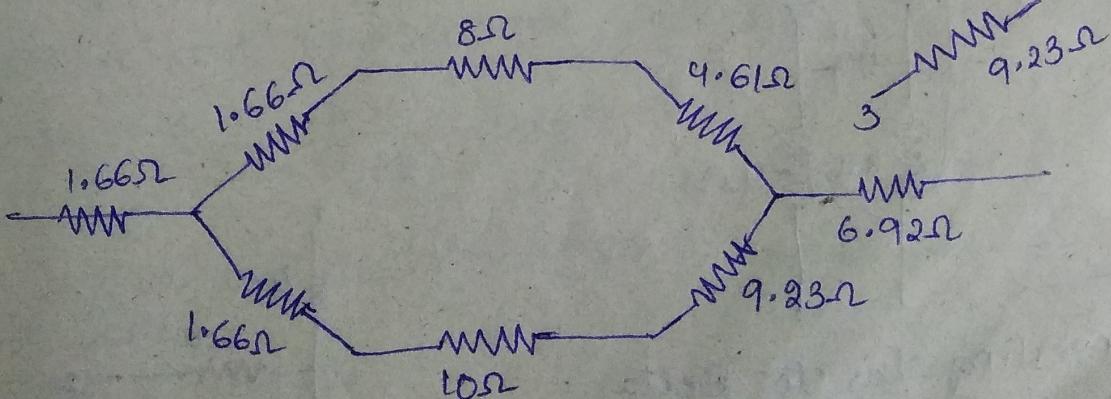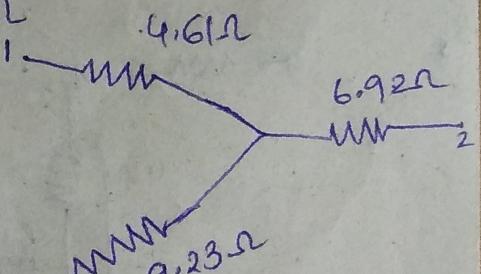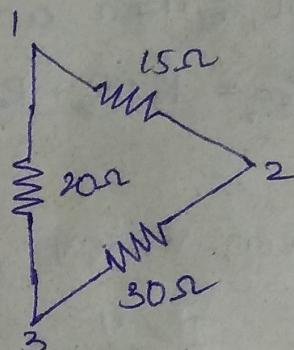
$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{30(20)}{15+30+20} = 9.23\Omega$$




$1.66\Omega$ ,  $8\Omega$  and  $4.61\Omega$  are in series connection
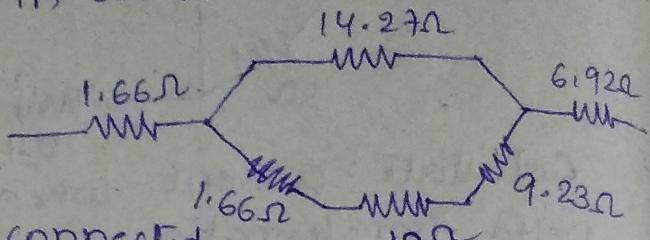
$$R_{eq} = 1.66 + 8 + 4.61 = 14.27\Omega$$




$1.66\Omega$ ,  $10\Omega$  and  $9.23\Omega$  are connected in series
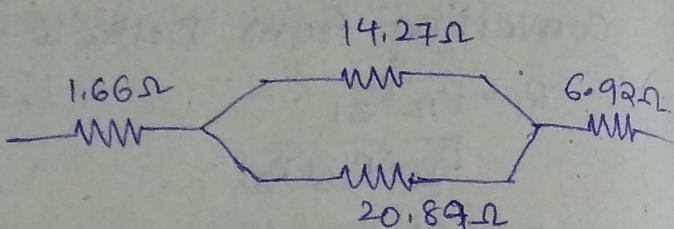
$$R_{eq} = R_1 + R_2 + R_3 = 1.66 + 10 + 9.23 = 20.89\Omega$$



$14.27\Omega$  and  $20.89\Omega$  are connected in parallel
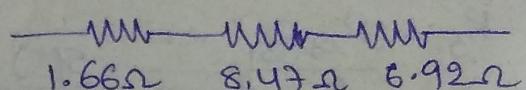
$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{14.27 \times 20.89}{14.27 + 20.89} = 8.47$$




$1.66\Omega$ ,  $8.47\Omega$  and  $6.92\Omega$  are connected in series

$$R_{eq} = R_1 + R_2 + R_3 = 1.66 + 8.47 + 6.92 = 17.05\Omega$$


Given  $V=30V$ ,  $R_{eq}=17.05$
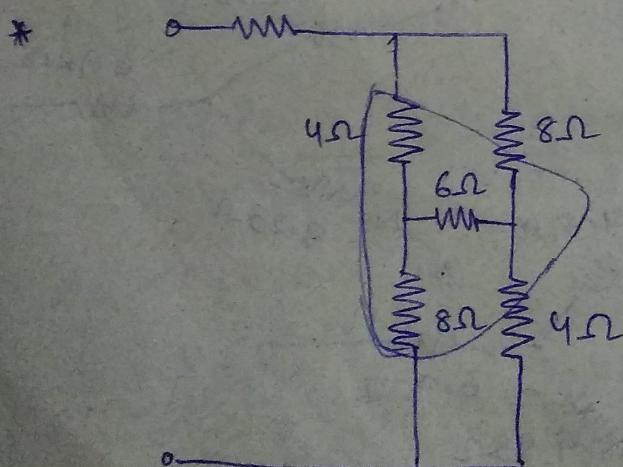
$$I = \frac{V}{R_{eq}} = \frac{30}{17.05} = 1.75A$$



Converting Star to Delta


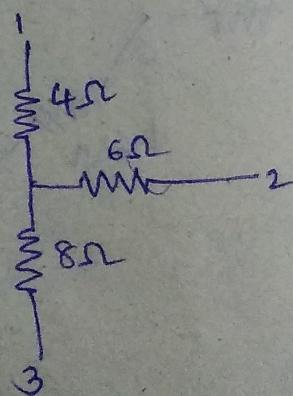
$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$



$$R_{12} = 4 + 8 + \frac{4(6)}{8} = 13\Omega$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1} = 6 + 8 + \frac{6(8)}{4} = 26\Omega$$
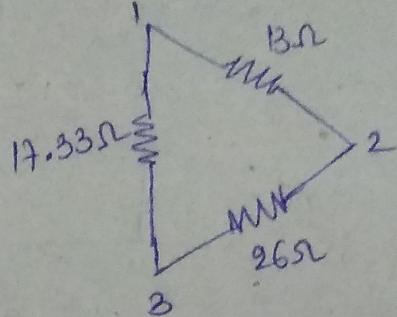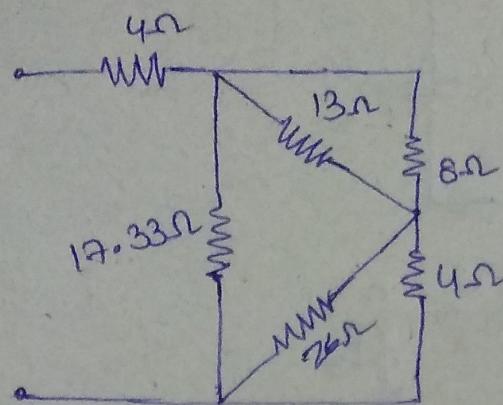
$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2} = 8 + 4 + \frac{8(4)}{6} = 17.33\Omega$$





13Ω and 8Ω are in parallel connection.

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{13(8)}{13 + 8} = 4.95\Omega$$

26Ω and 4Ω are in parallel connection 17.33Ω
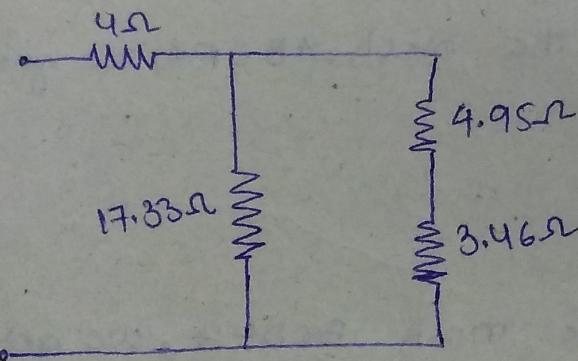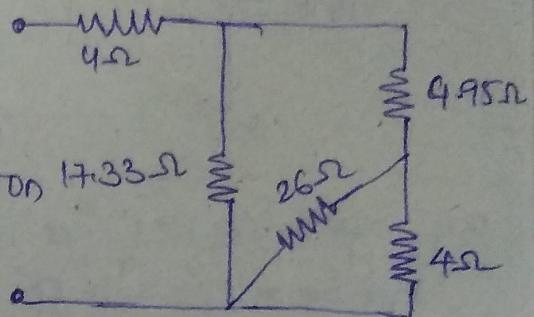
$$R_{eq} = \frac{4(26)}{4+26} = 3.46\Omega$$




4.95Ω and 3.46Ω are in series

$$R_{eq} = R_1 + R_2 = 4.95 + 3.46 = 8.41\Omega$$

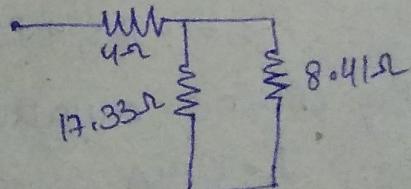
8.41Ω and 17.33Ω are connected in parallel

$$R_{eq} = \frac{8.41(17.33)}{8.41 + 17.33} = 5.66\Omega$$





5.66Ω and 4Ω are connected in series

$$R_{eq} = 5.66 + 4 = 9.66\Omega$$

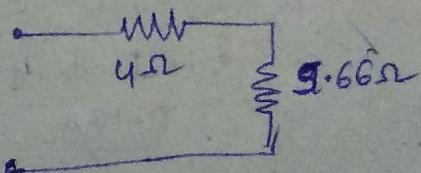

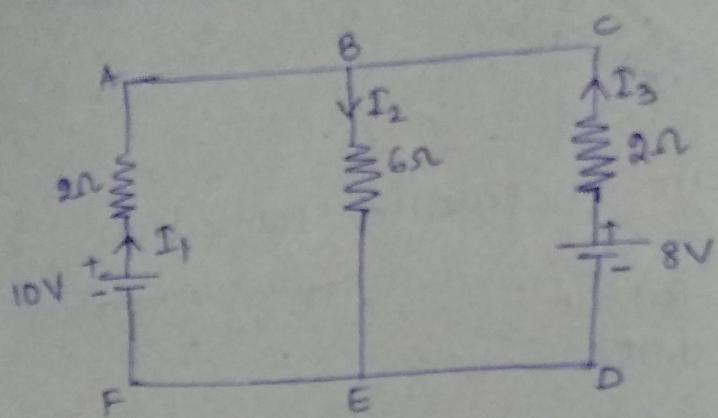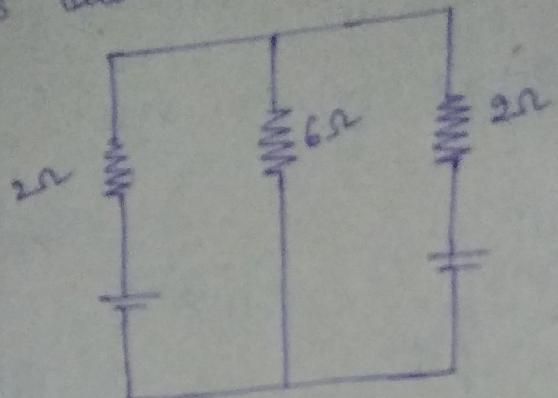\* find out all the branch currents by using Kirchoff's law



By applying KCL at node, we get

$$I_1 + I_3 = I_2 \quad \text{--- } ①$$

By applying KVL to the mesh ABCFA, we get

$$V_3 = V_1 + V_2$$

$$10 = 2I_1 + 6I_2$$

$$10 = 2I_1 + 6I_2 \quad \text{--- } ②$$

By applying KVL to the mesh BCDEB, we get

$$8 = 2I_3 + 6I_2 \quad \text{--- } ③$$

$$\text{Sub } I_2 - I_1 = I_3 \text{ in } ③$$

$$8 = 2(I_2 - I_1) + 6I_2$$

$$8 = -2I_1 + 8I_2 \quad \text{--- } ④$$

By solving equation ① & ④, we get


$$I_1 = 1.14 \text{ A} \quad I_2 = 1.28 \text{ A}$$

$$\begin{aligned} I_3 &= I_2 - I_1 \\ &= 1.28 - 1.14 \\ &= \underline{\underline{0.14 \text{ A}}} \end{aligned}$$

Q) Write the V-I

relation of R,L,C.

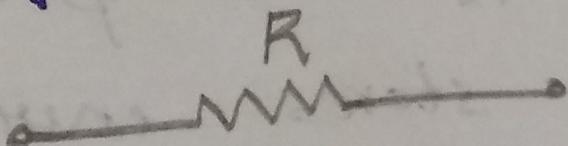Ans)  $\downarrow$  Resistance : It is the property of the material to oppose the flow of current. It is denoted by 'R'. It is measured by ohm. symbol is



It depends on the physical properties of the material

$$R = \frac{\rho L}{A}$$

$\rho$  - Resistivity

L - Length in metres

A - Area crosssection in square metres.

According to ohms law,

$$V = IR$$

$$I = V/R$$

$$I = GV$$

'G' is the conductance. The units are mho.

ohms law can be written as charge,

$$P \quad V = \frac{dq}{dt} R$$

The Power absorbed by the resistor is

$$P = VI = (IR)I = I^2 R = \frac{V^2}{R}$$

The energy lost is

$$W = \int_0^t pdt = pt = I^2 Rt = \frac{V^2}{R} t$$

where W is in Joules, power in watts,

I in Amperes, V in volts and t in seconds.

Inductance: It is the property of the material which stores energy as electro-magnetic field. It is denoted by

'L'. Its units are 'Henry'. symbol is  


the voltage is directly proportional to the change in current i.e

$$v \propto \frac{di}{dt}$$

$$v = L \frac{di}{dt}$$

$$di = \frac{1}{L} v dt$$

integrate on both sides

$$\int_0^t di = \frac{1}{L} \int_0^t v dt$$

$$i(t) - i(0) = \frac{1}{L} \int_0^t v dt$$

the current depends on the integral of voltage across the terminals and the initial current over the resistor.


The power absorbed by the inductor is

$$P = VI = L I \frac{di}{dt}$$

Energy lost is

$$W = \int_0^t P dt = \cancel{P t} = \int_0^t L I \frac{di}{dt} dt \\ = \frac{LI^2}{2}$$

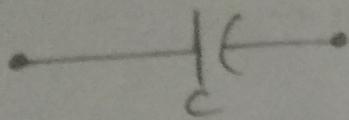Capacitance: It is the property of the material which stores energy as electrostatic field. It is denoted by 'C'. Its units are 'farad'. Its symbol is



$$C = \frac{Q}{V} = \frac{A}{V}$$

In capacitor, current is directly proportional to the change in voltage.

$$I = C \frac{dV}{dt}$$

$$\int_{0}^{t} dV = \frac{1}{C} \int_{0}^{t} I dt$$

$$V(t) - V(0) = \frac{1}{C} \int_{0}^{t} I dt$$

Power is

$$P = VI = V C \frac{dV}{dt}$$

Energy lost is


$$W = \int_{0}^{t} P dt = \int_{0}^{t} V C \frac{dV}{dt} dt$$

$$= \int_{0}^{t} V C dV$$

$$= \frac{CV^2}{2}$$


Capacitors are connected  
in Series
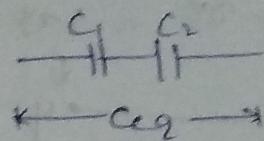
$$C_{eq} = \frac{C_1 + C_2}{C_1 + C_2} F$$



Capacitors are connected  
in parallel

$$C_{eq} = C_1 + C_2 + C_3 F$$

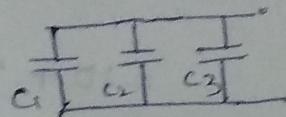

1)  $L_1 = 3H$   $L_2 = 5H$   $L_3 = 10H$

$$L_{eq} = 18H$$

Inductors in series & parallel

$$L_1 L_2 L_3$$

$$L_{eq} = (L_1 + L_2 + L_3) H$$

$L_{eq} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$

2)  $L_1 = 6H$   $L_2 = 3H$

$$L_{eq} = \frac{6 \times 3}{6 + 3}$$

$$L_{eq} = \frac{18}{9}$$

$$= 2H$$

3)  $C_1 = 25\mu F$   $C_2 = 10\mu F$


$$C_{eq} = 4.124 \mu F.$$

4)  $10\mu F$   $30\mu F$   $40\mu F$

$$C_{eq} = 10\mu F + 30\mu F + 40\mu F$$

$$= 80\mu F$$

5)  $C = 6\mu F$

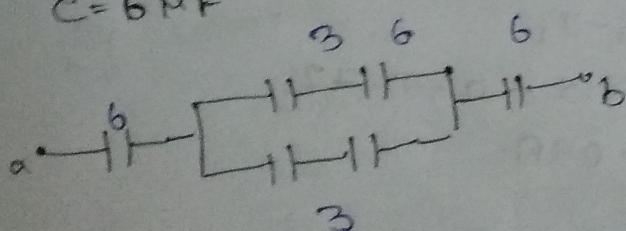

$$C = 2F$$

$$C_{eq} = \frac{6 \times 6}{6 + 6}$$

$$= 3$$

$$\frac{1}{C_{eq}} = \frac{1}{6} + \frac{1}{6} + \frac{1}{6}$$

$$\frac{1}{C} = \frac{3}{6}$$

$$\frac{1}{C} = \frac{1}{2} = 0.5$$