

Basic Electrical & Electronics Engineering [BEEE]

UNIT - I

Long Answer Questions:

- 1) Derivation of star-to-delta and delta-to-star.
- 2) Problems on series and parallel combination
- 3) Problems on source transformation.
- 4) Problems on nodal and mesh analysis.
- 5) Problems on star-to-delta and delta-to-star.
- 6) Write the V-I relation of R, L, C.

Short Answer Questions:

- 1) Define : a) Circuit b) Active & Passive elements c) Sources
d) Node, branch, mesh, loop. e) Linear & Non-linear circuits f) Balanced & Unbalanced circuits
g) Symmetrical & Asymmetrical circuits.

2) Define : charge, electric current, potential difference, power.

3) Define : a) Lumped & distributed elements.

b) Uni-lateral & bilateral circuits.

c) Time Variant & Time invariant circuits.

4) Define resistance, inductance and capacitance. Write their V-I relation.

5) Define Ohm's law. What are its limitations & applications?

6) Define KVL and KCL with an example.

7) Define series and parallel circuits with an example.

8) Draw the diagrams of star and delta connections.

9) Define Admittance, Impedance, Susceptance & Conductance

UNIT - II

10) Explain about Voltage division rule & Current division rule

Long Answer Questions:

1) DC theorems (all 5).

2) AC through R, L, C circuits

- 3) AC through RL, RC and RLC circuits.
- 4) Problems on RL, RC and RLC series circuit.

Short Answer Questions:

- 1) All definitions of $1-\phi$ AC circuits.
- 2) Statements & procedures of all 5 theorems.
- 3) Differences between AC and DC.

UNIT - II (PART-A)

Long Answer Questions:

- 1) Write the relation between line & phase values and power expression for balanced $3-\phi$ star connection.
- 2) Write the relation between line & ~~phi~~ phase values and power expression for balanced $3-\phi$ delta connection.

Short Answer Questions:

- 1) All definitions of $3-\phi$ AC circuits.
- 2) Difference between star and delta connections.
- 3) Advantages of $3-\phi$ AC circuits.

UNIT - II (PART-B)

Long Answer Questions:

- 1) Explain the working of P-N junction diode.
(Or)

Explain the V-I characteristics of P-N junction diode.

- 2) Differences between Ideal & Practical Diodes.
- 3) Effect of temperature on P-N Junction diode.

Short Answer Questions:

- 1) Symbols of PN, Zener and BJT.
- 2) What is diode current equation.

- 3) Characteristics of PN, Zener diodes.
- 4) What is no-bias condition.
- 5) Explain: Diode as a switch.
- 6) Comparison of V-I characteristics of PN and Zener diodes.
- 7) Advantages, disadvantages and applications of PN, Zener diode.

UNIT-IV (PART-A)

Short Answer Questions:

- 1) Explain the block diagram of RPS.
- 2) What is a rectifier? What are the types of rectifiers?
- 3) Advantages & disadvantages of all types of rectifiers.
- 4) All definitions.

Long Answer Questions:

- 1) Explain the working of half-wave rectifier with necessary sketches and parameters.
- 2) Explain the working of centre-tap full wave rectifier with necessary sketches and parameters.
- 3) Explain the working of bridge rectifier with necessary sketches and parameters.
- 4) Differences amongst half-wave, centre-tap and ~~br~~ bridge rectifiers.

UNIT-IV (PART-B)

Long Answer Questions:

- 1) Explain the working of Zener diode.
- 2) Explain the working of Zener diode as voltage regulator.
- 3) Difference between breakdown mechanisms [Zener breakdown v/s avalanche breakdown].

Short Answer Questions:

- 1) Define Zener diode.

- 2) Advantages, disadvantages and applications of Zener diode.
- 3) Differences between P-N junction diode and Zener diode.

UNIT - 2

Long Answer Questions:

- **1) Explain the CB configuration.
- **2) Explain the CE configuration.
- **3) Explain the CC configuration.
- 4) Explain the need of biasing and what are the types of biasing techniques.
- 5) DC and AC load line.

Short Answer Questions:

- 1) Define transistor.
- 2) Define the construction of the transistor (P-N-P, N-P-N).
- 3) Define the operation of the transistor.
- 4) Relationship between α , β , γ .
- 5) Define early effect and punch through effect.
- 6) Advantages & disadvantages of transistor.
- 7) Define thermal runaway.
- 8) Explain the working of transistor as an amplifier.
- 9) Why BJT is called as Current Controlled device & Explain.
- 10) Derive the expressions for Transistor leakage currents.
- 11) Problems on α , β & γ .
- 12) Compare CB, CE & CC configurations.